

Table of Contents

ELEC 4700 Assignment 4 - Circuit Modeling	2
Q1.....	2
Q2.....	8
Q3.....	8
Q3 a) Formulation.....	9
Q3 b) Programing i.....	9
Q3 b) ii.....	10
Q3 b) iii.....	12
Q4 Transient Circuit Simulation	14
Q4 a).....	15
Q4 b).....	15
Q4 c)	15
Q4 d).....	15
Q4 d) Input signal A:.....	16
Q4 d) Input signal B:.....	18
Q4 d) Input signal B (few other frequencies):.....	19
Q4 d) Input signal C.....	22
Q4 d) v.....	24
Q4 d) v Comment.....	26
Q5 Circuit with Noise	26
Q5 vi	28
Q5 vi. Comment	32
Q5 vii	32
Q5 vii Comment	35
Q6 Non-linearity.....	35
Q6 Implementation.....	36
Helper functions.....	39

ELEC 4700 Assignment 4 - Circuit Modeling

Student: Samuel (Wendi) Zhu

Student Number: 101088968

Date: 4/7/2022

```
% Clear all
clear
clearvars
clearvars -global
close all
format shorte

% Make plot prettier
% set(0,'DefaultFigurewindowstyle','docked')
set(0,'defaultaxesfontsize',14)
set(0,'defaultaxesfontname','Times New Roman')
set(0,'DefaultLineLinewidth', 1);
```

Q1

Using a fixed bottled neck value and the simulation code for assignment 3, do a voltage sweep of the device from 0.1V to 10V and model the current-voltage characteristics.

```
% Global variables
global Const      % constants module that holds all the constants
global x y        % arrays for the current electrons positions: 1 row, column for current position
global xp yp      % arrays for the previous electrons positions: 1 row, column for previous
position
global vx vy      % arrays for current electrons velocities: 1 row, column for current velocity
global ax ay      % scalars for electron acceleration in x and y direction
global limits      % Limits for the plot
global boxes; % matrix for the boxes: n rows, and 4 columns for [x y w h]
% Initialize global constants
% Electron charge
Const.q_0 = 1.60217653e-19; % C
% Rest mass
Const.m0 = 9.1093837015e-31; % KG
% Effective mass of electrons
Const.mn = 0.26*Const.m0; % KG
% Boltzmann constant
Const.kb = 1.38064852e-23; % m^2 * kg * s^-2 * K^-1

% Initialize the region size 200nm X 100nm
Region.x = 200e-9;
Region.y = 100e-9;
limits = [0 Region.x 0 Region.y]; % plot limit
% Initialize the temperature
T = 300; % K
% Initialize the mean time between collision
Tmn = 0.2e-12; % 0.2ps
```

```

% Define the dimension
L = Region.x * 10^9; % Length in nm
W = Region.y * 10^9; % width in nm
boxLF = 0.3; % Fraction of the length of the box
boxWF = 0.4; % Fraction of the width of the box
Lb = boxLF*L; % Length of the box in nm
Wb = boxWF*W; % Width of the box in nm
deltaxY = 0.02*L; % Assume deltax = deltay in nm
% Calculate the dimension of solution matrix
nx = (L/deltaxY);
ny = (W/deltaxY);

% Number of sweep points for the voltage
nSweep = 10;
vecVoltage = linspace(0.1, 10, nSweep); % Generate the voltage vector
vecCurrent = zeros(1, nSweep); % vector for holding the current
% vector for different deltaT to adjust the time to reach steady state
vecDeltaT = linspace(12e-14, 3e-14, nSweep);

% Loop through the different voltages
for ivolt = 1:length(vecVoltage)
    % Define the voltages
    voltagex0 = vecVoltage(ivolt); % Voltage at X=0
    voltagex1 = 0; % Voltage at X=L
    % Define deltaT to reach steady state sooner
    deltaT = vecDeltaT(ivolt);

    % Step 1: Calculate the E field
    % calculate the meshgrid
    [X,Y] = meshgrid(linspace(0,L,nx), linspace(0,W,ny));
    % Declare the matrix for conductivity: Sigma(y,x)
    matrixSigma = ones(ny, nx); % Dimension: ny times nx
    xIndexBox = ceil((L-Lb)/(2*deltaxY)); % Find the starting x index for the box
    LbIndexRange = ceil(Lb/deltaxY); % Index range for the length of the box
    WbIndexRange = ceil(Wb/deltaxY); % Index range for the width of the box
    % Assign the region for the box
    matrixSigma(1:WbIndexRange, xIndexBox:xIndexBox+LbIndexRange) = 10^-2;
    matrixSigma(ny-WbIndexRange:ny, xIndexBox:xIndexBox+LbIndexRange) = 10^-2;
    % Declare the matrix for voltage V(y,x)
    matrixV = zeros(ny, nx); % Dimension: ny times nx
    % Declare the G matrix and F vector: GV = F
    G = zeros(nx*ny, nx*ny);
    F = zeros(nx*ny, 1);
    % Construct the G matrix and F vector
    for ix = 1:nx
        for iy = 1:ny
            % Calculate the index
            n = mappingEq(ix, iy, ny);
            % Check for the boundary
            if ix==1 || ix==nx || iy ==1 || iy==ny
                G(n,n) = 1;
                % Boundary condition for x
                if ix == 1
                    F(n,1) = voltagex0; % v at x = 0

```

```

        elseif ix == nx
            F(n,1) = voltageX1; % and v at x = L
        elseif iy == 1
            nyp = mappingEq(ix, iy+1, ny); % dv/dy=0 at y=0
            G(n,nyp) = -1;
        elseif iy == ny
           nym = mappingEq(ix, iy-1, ny); % dv/dy=0 at y=w
            G(n, nym) = -1;
        end
    else
        % calculate the sigma
        sigmaxp = (matrixSigma(iy,ix) + matrixSigma(iy,ix+1))/2;
        sigmaxm = (matrixSigma(iy,ix) + matrixSigma(iy, ix-1))/2;
        sigmayp = (matrixSigma(iy,ix) + matrixSigma(iy+1, ix))/2;
        sigmaym = (matrixSigma(iy,ix) + matrixSigma(iy-1, ix))/2;
        % calculate mapping index
        nxp = mappingEq(ix+1, iy, ny); % index for v(i+1,j)
        nxm = mappingEq(ix-1, iy, ny); % index for v(i-1,j)
        nyp = mappingEq(ix, iy+1, ny); % index for v(i,j+1)
       nym = mappingEq(ix, iy-1, ny); % index for v(i,j-1)
        % Setup the G matrix
        G(n,n) = -(sigmaxp+sigmaxm+sigmayp+sigmaym)/deltaxy^2;
        G(n, nxp) = sigmaxp/deltaxy^2;
        G(n, nxm) = sigmaxm/deltaxy^2;
        G(n, nyp) = sigmayp/deltaxy^2;
        G(n, nym) = sigmaym/deltaxy^2;
    end
end
% Solve for v from GV = F
V = G\F;
% Map back to the 2D region
for iMap = 1:nx*ny
    % calculate the index for the 2D region
    ix = ceil(iMap/ny);
    iy = mod(iMap, ny);
    if iy == 0
        iy = ny;
    end
    % Assign the value
    matrixv(iy, ix) = V(iMap);
end
% Solve the electric field
[Ex, Ey] = gradient(-matrixv);
Ex = Ex/(deltaxy * 10^-9); % convert to V/m
Ey = Ey/(deltaxy * 10^-9); % convert to V/m

% Step 2: Calculate the acceleration field
% Initialize the number of "super" electrons
numE = 1000;
% Number of simulation steps
numSim = 1000;
% Boundary mode: specular(0) or diffusive(1)
boundaryMode = 0;

```

```

% Add the boxes
numBox = AddObstacles(boxLF, boxWF, Region);
% To find the current, the following steps are performed:
% 1) calculate the total area
areaA = Region.x * Region.y; % m^2
areaA = areaA * 100^2; % cm^2
% 2) calculate the total electrons in the area assuming electron
% concentration is 10^15 cm^-2
totalE = 10^15 * areaA; % total electrons
% 3) Find the charge per "Super Electron", where "Super Electron" is the
% particle in this simulation
numEPersuperE = totalE/numE; % number of electron per super electron
superECharge = -Const.q_0 * numEPersuperE; % Charge per super electron
% 4) The current can be found by counting the net number of super electrons

% Initialize acceleration for each electron
ax = zeros(1, numE); % Acceleration in x
ay = zeros(1, numE); % Acceleration in y
% Calculate the acceleration field: a = Force/mass = q*E/mass
accFieldX = -Const.q_0 * Ex / (Const.mn);
accFieldY = -Const.q_0 * Ey / (Const.mn);

% Add the electrons
AddElectrons_WithBox(numE, Region, T, numBox);
% Calculate the scattering probability
Pscat = 1-exp(-deltaT/Tmn);

% Super electron count for current calculation
% Count on left side x=0. +1 flow right, -1 flow left
countECurrent = 0; % Hold the super electron count

% Step 3: Loop for simulation
for isim = 1:numSim
    % Store the current positions
    xp = x;
    yp = y;
    % Calculate the future positions: x = x0 + vx*t + 1/2*ax*t^2
    x = x + vx * deltaT + 1/2 * ax * deltaT^2;
    y = y + vy * deltaT + 1/2 * ay * deltaT^2;
    % Calculate the future velocity: vx = ax*t
    vx = vx + ax*deltaT;
    vy = vy + ay*deltaT;

    % Reset the super electron count
    countECurrent = 0;

    % Loop through all the particles
    for iE=1:numE
        % flag for invalid position
        bInvalid = false;
        % Step 1 - Check for boundary
        % Check for invalid x position
        if x(iE) <= 0
            x(iE) = Region.x; % Appear on right

```

```

xp(iE) = x(iE);
bInvalid = true;
% Update the electron count for current calculation
countECurrent = countECurrent-1; % -1 flow left
elseif x(iE) >= Region.x
    x(iE) = 0; % Appear on left
    xp(iE) = x(iE);
    bInvalid = true;
    % Update the electron count for current calculation
    countECurrent = countECurrent+1; % +1 flow right
end
% Check for invalid y position
if y(iE) <= 0
    bInvalid = true;
    y(iE) = 0;
    % Check for boundary mode
    if boundaryMode == 0 % Specular boundary
        vy(iE) = -vy(iE);
    else % Diffusive boundary
        vy(iE) = abs(sqrt(Const.kb*T/Const.mn).*randn()); % positive vy
    end
elseif y(iE) >= Region.y
    y(iE) = Region.y;
    bInvalid = true;
    % Check for boundary mode
    if boundaryMode == 0 % Specular boundary
        vy(iE) = -vy(iE);
    else % Diffusive boundary
        vy(iE) = -abs(sqrt(Const.kb*T/Const.mn).*randn()); % negative vy
    end
end
% Step 2: Check for boxes
for iBox = 1:numBox
    % Retrieve box info
    boxX1 = boxes(iBox, 1);
    boxX2 = boxes(iBox, 1)+boxes(iBox, 3);
    boxY1 = boxes(iBox, 2);
    boxY2 = boxes(iBox, 2)+boxes(iBox, 4);
    % Check if the particle is inside a box
    if (x(iE)>=boxX1 && x(iE)<=boxX2 && y(iE)>=boxY1 && y(iE) <= boxY2)
        bInvalid = true; % Invalid position
        % Check for x position
        if xp(iE) <= boxX1 % Coming from left side
            x(iE) = boxX1;
            % Check for boundary mode
            if boundaryMode == 0 % Specular boundary
                vx(iE) = -vx(iE);
            else % Diffusive boundary
                vx(iE) = -abs(sqrt(Const.kb*T/Const.mn).*randn())); % negative vx
            end
        elseif xp(iE) >= boxX2 % Coming from right side
            x(iE) = boxX2;
            % Check for boundary mode
            if boundaryMode == 0 % Specular boundary

```

```

        vx(iE) = -vx(iE);
    else % Diffusive boundary
        vx(iE) = abs(sqrt(Const.kb*T/Const.mn).*randn()); % positive vx
    end
end
% Check for y position
if yp(iE) <= boxY1 % Coming from bottom
    y(iE) = boxY1;
% Check for boundary mode
if boundaryMode == 0 % Specular boundary
    vy(iE) = -vy(iE);
else % Diffusive boundary
    vy(iE) = -abs(sqrt(Const.kb*T/Const.mn).*randn()); % negative vy
end
elseif yp(iE) >= boxY2 % Coming from top
    y(iE) = boxY2;
% Check for boundary mode
if boundaryMode == 0 % Specular boundary
    vy(iE) = -vy(iE);
else % Diffusive boundary
    vy(iE) = abs(sqrt(Const.kb*T/Const.mn).*randn()); % positive vy
end
end
% Break the loop for box
break;
end
end
% Step 3: Check for scattering
if ~bInvalid && Pscat > rand()
    % Rethermalize
    vx(iE) = sqrt(Const.kb*T/Const.mn).*randn();
    vy(iE) = sqrt(Const.kb*T/Const.mn).*randn();
end
% Step 4: Find acceleration
% Find the corresponding index for the acceleration field
indexX = ceil(x(iE)/(deltaxY*10^-9));
indexY = ceil(y(iE)/(deltaxY*10^-9));
% Check for invalid index
if indexX <= 0
    indexX = 1;
end
if indexY <= 0
    indexY = 1;
end
% Assign the acceleration of the electron
ax(iE) = accFieldX(indexX);
ay(iE) = accFieldY(indexY);
end
end

% calculate the current
vecCurrent(ivolt) = superECharge*countECurrent/deltaT;

end

```

```
% Plot the current versus voltage characteristics
figure(1)
plot(vecVoltage, vecCurrent, "-b.")
title("Current - Voltage Characteristics")
xlabel("Voltage (V)")
ylabel("Current (A)")
% Do the linear fit for determining resistance value of the device
slopeRfit = vecVoltage(:)\vecCurrent(:);
Rfit = vecVoltage(:)*slopeRfit;
hold on;
plot(vecVoltage, Rfit, "r-.")
legend("Simulation Data", "Linear Fit Line", "Location", "southeast")
grid on
snapnow
```

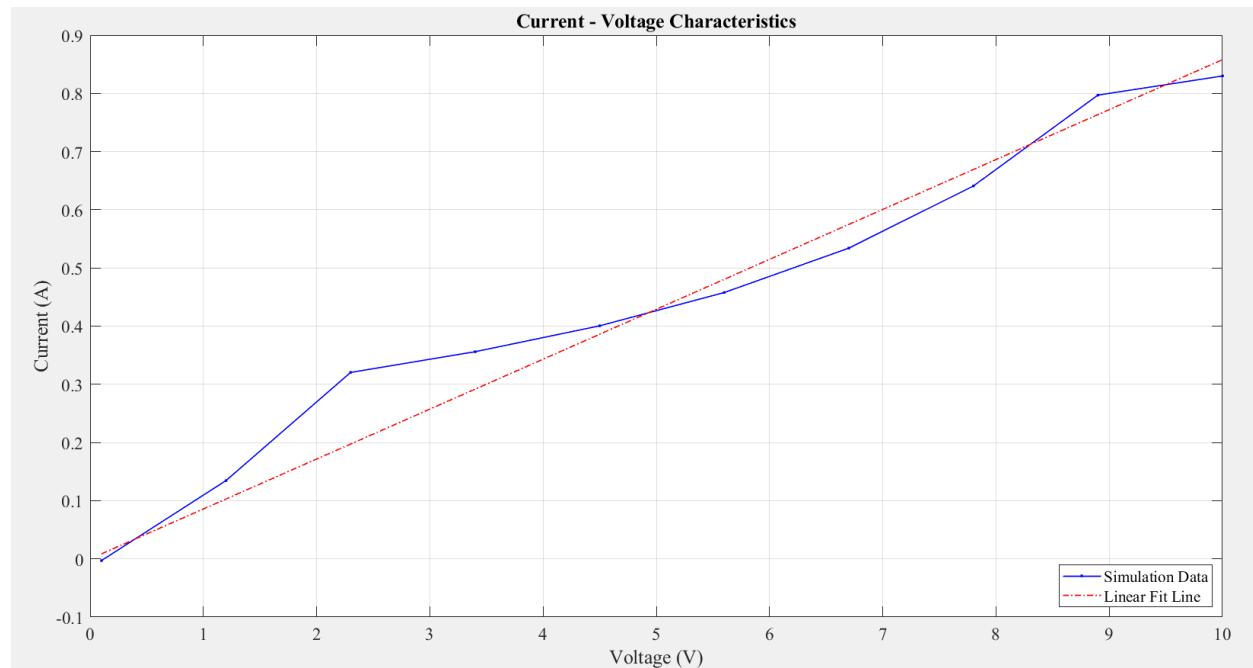


Figure 1 Current vs Voltage Characteristics for determining resistance value of the device

Q2

Use a linear fit to determine the resistance value pf the device and use this value as R3

```
% Calculate the R3 value
R3 = 1/slopeRfit; % Ohm
% Print the linear fitted value
fprintf("Resistance value from linear fit: R3 = " + R3 + " Ohms.\n")
```

Resistance value from linear fit: R3 = 11.6555 Ohms.

Q3

Report on the work done in PA 9 (PA 7).

```
% Declare some component values
R1 = 1; % Ohm
C = 0.25; % F
R2 = 2; % Ohm
L = 0.2; % H
alpha = 100;
R4 = 0.1; % Ohm
RO=1000; % Ohm

% Declare the vectors
vectorV = zeros(9, 1); % solution vector: [N1, N2, N3, N4, N5, I1, IL, I3, I4]
vectorF = zeros(9, 1); % F vector: F(1) = VIN
```

Q3 a) Formulation

Please see the Appendix A for the differential equations that represent the network and the derivation for the C and G matrix.

```
% Create the C, G matrices
% Declare the C matrix
matrixC = [0, 0, 0, 0, 0, 0, 0, 0, 0;
            C, -C, 0, 0, 0, 0, 0, 0, 0;
           -C, C, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, -L, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0];

% Declare the G matrix
matrixG = [1,      0,      0,      0,      0,      0,      0,      0;
            1/R1,   -1/R1,   0,      0,      0,      1,      0,      0;
           -1/R1,   1/R1+1/R2, 0,      0,      0,      0,      1,      0;
            0,      1,      -1,      0,      0,      0,      0,      0;
            0,      0,      0,      0,      0,      0,      -1,      1;
            0,      0,      -1/R3,   0,      0,      0,      0,      1;
            0,      0,      0,      1/R4,   -1/R4,   0,      0,      0;
            0,      0,      0,      1,      0,      0,      0,      -alpha;
            0,      0,      0,      -1/R4,   1/R4+1/RO, 0,      0,      0];
```

Q3 b) Programming i.

DC sweep input voltage from -10V to 10V and plot V0 and V3 (N3).

```
simStep = 21; % Simulation steps
V1 = linspace(-10, 10, simStep); % vector for input voltages
V0 = zeros(simStep, 1); % vector for holding the output voltage
V3 = zeros(simStep, 1); % vector for holding the voltage at V3
% Loop for the DC simulation
for isim = 1:simStep
```

```

% Setup the F vector
vectorF(1) = v1(isim); % Stepup the input voltage
% Find the solution
vectorV = matrixG\vectorF;
% Save answers
Vo(isim) = vectorV(5); % Save Vout
V3(isim) = vectorV(3); % Save V3
end
% Plot the DC simulation
figure(2)
plot(v1, Vo, "-b.")
hold on
plot(v1, V3, "-r.")
title("DC simulation")
xlabel("vin (V)")
ylabel("vout and V3 (V)")
legend("Vout", "V3")
grid on;
snapnow

```

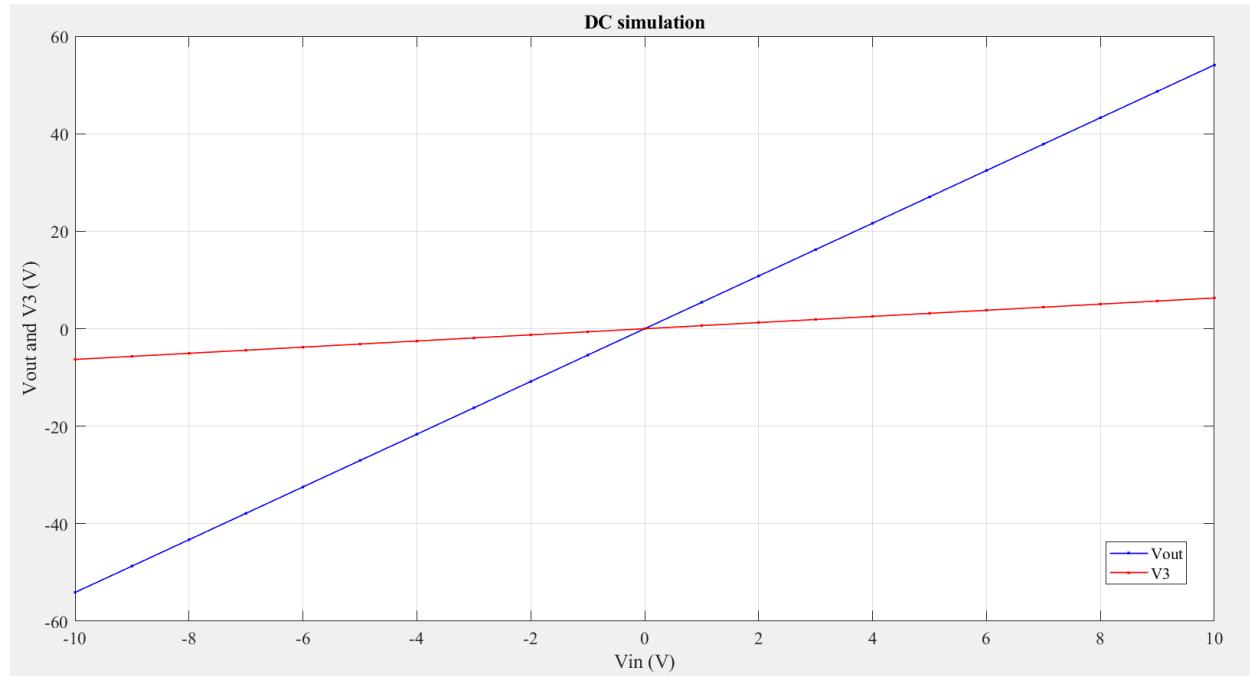


Figure 2 DC simulation for sweep the input voltage from -10 V to 10 V

Q3 b) ii.

For the AC case, plot Vo as a function of omega also plot the gain v_o/v_1 in dB.

```

simSteps = 100; % simulation steps
vin = 1; % value for input voltage
vectorF(1) = vin; % Setup the input voltage
omega = linspace(1, 100, simSteps); % vector for frequencies
vo = zeros(simSteps, 1); % vector store the output voltages

```

```

v3 = zeros(simStep, 1); % vector for holding the voltage at v3

% Loop for simulation
for isim = 1:simSteps
    w = omega(isim); % Retrieve the simulation frequency
    % Construct the G+jwC matrix
    matrixGC = matrixG + 1j*w*matrixC;
    % Find the solution
    vectorV = matrixGC\vectorF;
    % Save answers
    Vo(isim) = abs(vectorV(5)); % Save Vout
    v3(isim) = abs(vectorV(3)); % Save V3
end
% Plot Vo as a function of omega
figure(3)
plot(omega, Vo, "-b.");
hold on
plot(omega, v3, "-r.");
title("Vo as a function of omega")
xlabel("Frequency omega (rad/s)")
ylabel("Vout (V)")
legend("Vout", "V3")
grid on
snapnow

% Plot the gain Vo/V1 in dB
figure(4)
gain = 20.*log10(vo ./ vin); % calculate the gain in dB
plot(omega, gain);
title("Gain Vo/V1 in dB versus omega")
xlabel("Frequency omega (rad/s)")
ylabel("Gain (dB)")
grid on
snapnow

```

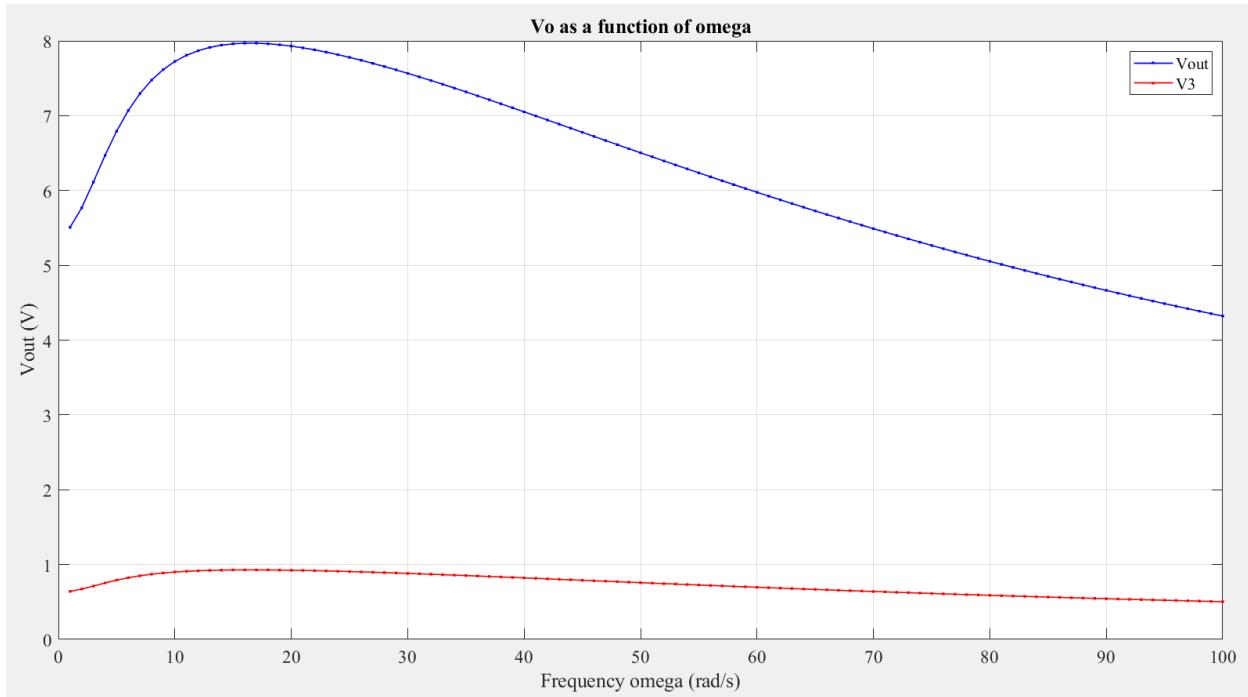


Figure 3 V_o as a function of ω

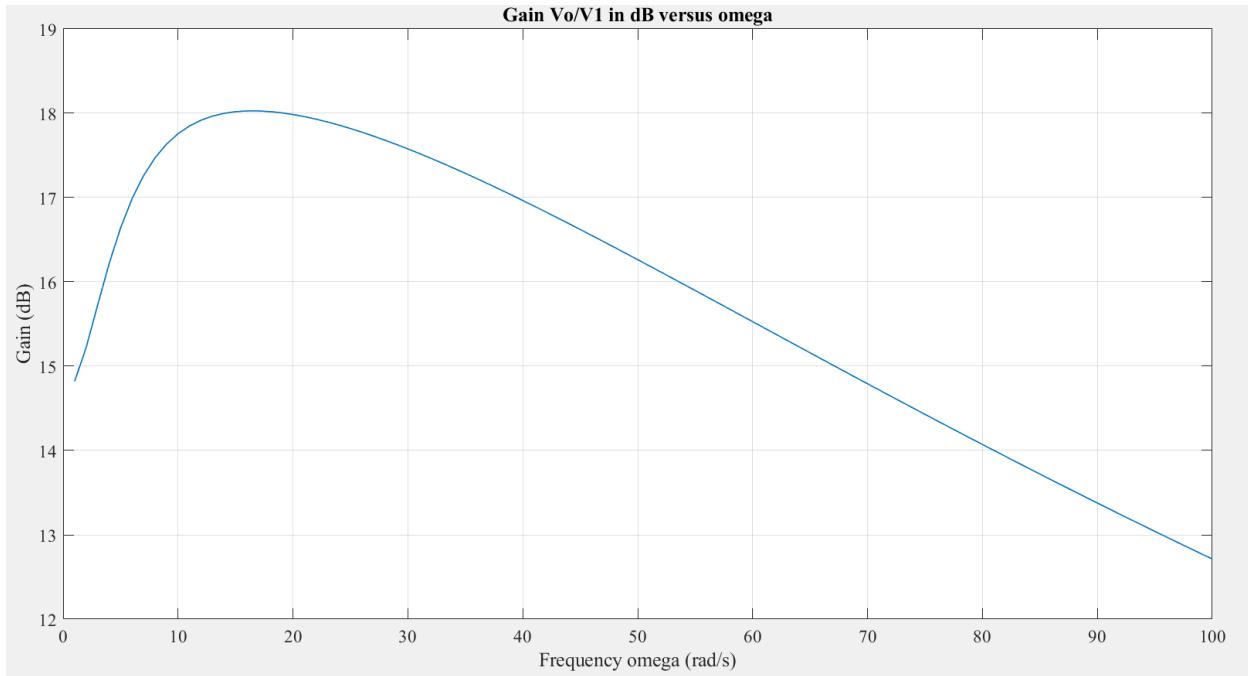


Figure 4 Gain V_o/V_1 in dB versus ω

Q3 b) iii.

For the AC case, plot the gain as function of random perturbations on C using a normal distribution with std=.05 at omega = pi. Do a histogram of the gain.

```

simSteps = 1000; % simulation steps
omega = pi;
std = 0.05; % Standard deviation of the normal distribution
randomC = std .* randn(simSteps, 1)+C; % vector store the random C
Vo = zeros(simSteps, 1); % vector store the output voltages
Vin = 10; % Value for input voltage
vectorF(1) = Vin; % Setup the input voltage

% Plot the normal distribution of C
nbins = 10; % Number of bins for the histogram
figure(5)
histogram(randomC, nbins);
title("Distribution of C")
xlabel("C (F)")
ylabel("Number")
grid on
snapnow

% Loop through the random C
for isim=1:simSteps
    C = randomC(isim); % Retrieve the C value
    % Reconstruct the C matrix
    matrixC = [0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               C, -C, 0, 0, 0, 0, 0, 0, 0, 0;
               -C, C, 0, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, -L, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0];
    % Construct the G+jwC matrix
    matrixGC = matrixG + 1j*omega*matrixC;
    % Find the solution
    vectorV = matrixGC\vectorF;
    % Save answers
    Vo(isim) = abs(vectorV(5)); % Save Vout
end

% Plot the distribution of gain
figure(6)
gain = Vo ./ Vin; % calculate the gain
histogram(gain, nbins);
title("Distribution of Gain")
xlabel("Vo/Vi (V/V)")
ylabel("Number")
grid on
snapnow

```

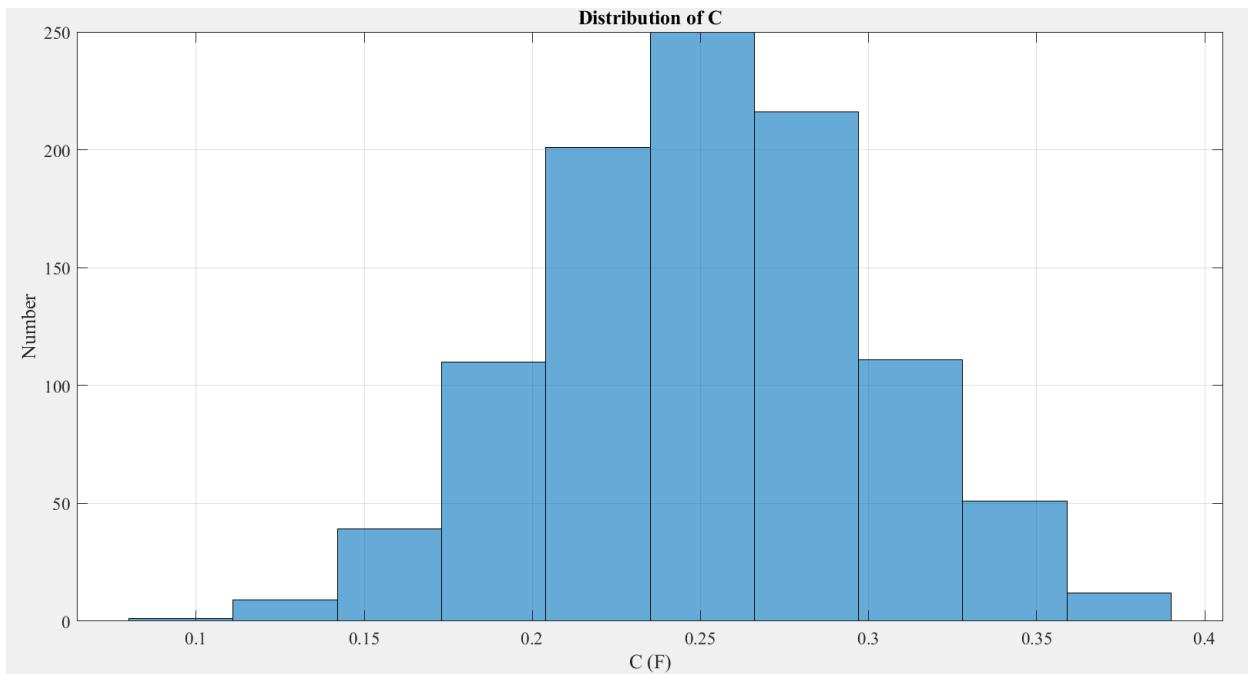


Figure 5 Distribution of C

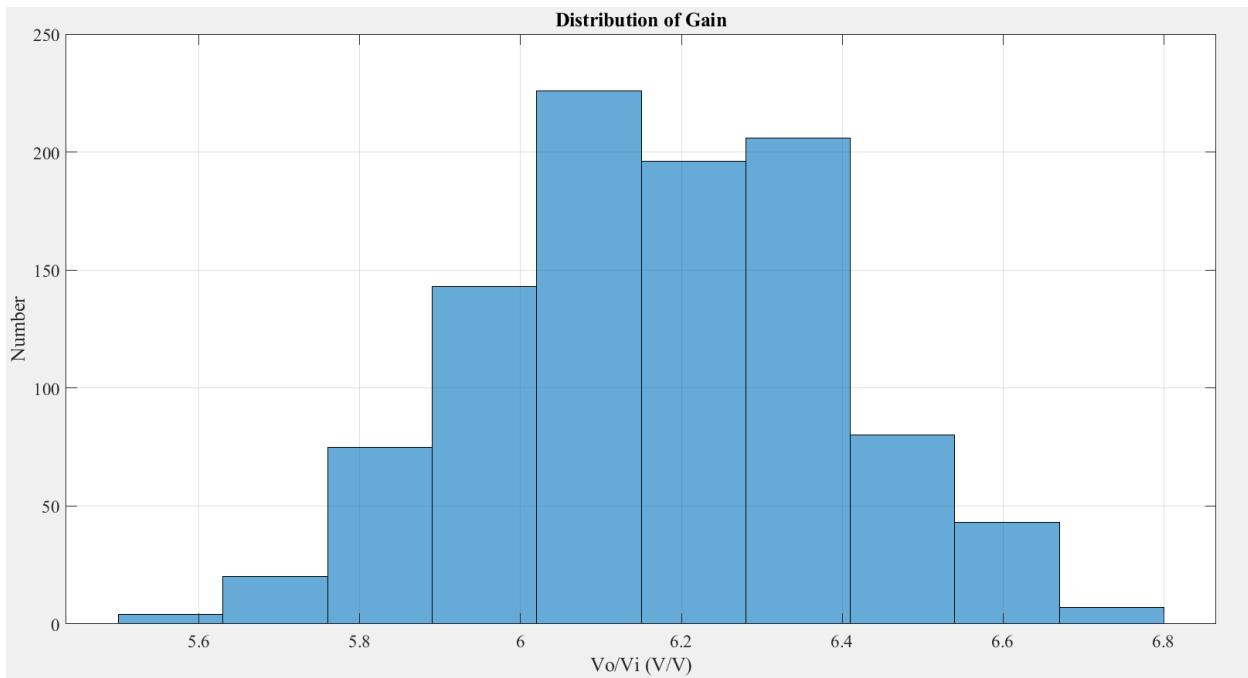


Figure 6 Histogram of the gain as random perturbations on C

Q4 Transient Circuit Simulation

The circuit can be represented in the time domain as:

$$C \frac{dV}{dt} + GV = F$$

Q4 a)

By inspection what type of circuit is this?

By inspection, the circuit is an LRC circuit, and the circuit models an amplifier. The circuit is linear since it does not contain any nonlinear components yet.

Q4 b)

What sort of frequency response would you expect?

When the frequency is high, the impedance for L will be large, and the output voltage will be low. This suggest that the circuit has an overall low pass response. However, the simulation waveform of Gain versus omega shows that the gain is also relatively low at the near DC frequency. Therefore, strictly speaking, the frequency response of the circuit is bandpass response.

Q4 c)

The derivation for the formulation in time domain is shown as follow:

Solving MNA Time Domain (implicit):

$$\begin{aligned} \therefore C \frac{dV}{dt} + CV &= F(t) \\ C \frac{V_j - V_{j-1}}{\Delta t} + GV_j &= F(t_j) \\ C \frac{V_j}{\Delta t} + GV_j &= C \frac{V_{j-1}}{\Delta t} + F(t_j) \\ \left(\frac{C}{\Delta t} + G \right) V_j &= C \frac{V_{j-1}}{\Delta t} + F(t_j) \end{aligned}$$

Let define $A = \frac{C}{\Delta t} + G$, then

$$\begin{aligned} AV_j &= C \frac{V_{j-1}}{\Delta t} + F(t_j) \\ \therefore V_j &= A^{-1} \left[C \frac{V_{j-1}}{\Delta t} + F(t_j) \right] \end{aligned}$$

The derived equation is:

$$V_j = A^{-1} \left[C \frac{V_{j-1}}{\Delta t} + F(t_j) \right]$$

Where $A = \frac{C}{\Delta t} + G$.

Q4 d)

Write a Matlab program that can simulate the circuit. Simulate for 1s and use 1000 steps.

```
simTime = 1; % Simulate for 1 second
simSteps = 1000; % Use 1000 steps
% Calculate the deltaT
```

```

deltaT = simTime/simSteps; % second/step
% Declare the time vector
vecTime = linspace(0,1,simSteps);

```

Q4 d) Input signal A:

A step that transitions from 0 to 1 at 0.03s.

iii. Plot the input Vin and output V as the simulation progresses.

iv. After the simulation is completed, use the fft() and fftshift() functions to plot the frequency of the input and output signals.

```

% Declare the input for a step from 0 to 1 at 0.03s
vecInputV = zeros(1, simSteps);
vecInputV(0.03*simSteps:simSteps) = 1;
% Hold the output vector
vecOutputV = zeros(1, simSteps);

% Initialize the V and F vector
vectorV = zeros(9, 1); % solution vector: [N1, N2, N3, N4, N5, I1, IL, I3, I4]
vectorF = zeros(9, 1); % F vector: F(1) = VIN
% Construct the A matrix
matrixA = matrixC/deltaT + matrixG;

% Loop through the simulation
for isim = 1:simSteps
    % Update the F vector
    vectorF(1) = vecInputV(isim);
    % Update the V vector
    vectorV = matrixA^-1 * (matrixC * vectorV / deltaT + vectorF);
    % Save the output voltage
    vecOutputV(isim) = vectorV(5);

    % % Plot the input Vin and output V as the simulation progresses
    % figure(7)
    % plot(vecTime(1:isim), vecInputV(1:isim), "-r.") % Vin versus time
    % hold on
    % plot(vecTime(1:isim), vecOutputV(1:isim), "-b.") % Vo versus time
    % hold off
    % title("Transient simulation for a step input")
    % xlabel("Time (s)")
    % ylabel("Voltage (V)")
    % legend("Vin versus time", "vo versus time", "Location", "southeast")
    % grid on
    % % Pause for a while
    % pause(0.002)
end

% Plot of completed transient simulation for step input
figure(7)
% Time domain plot
subplot(1,2,1)

```

```

plot(vecTime, vecInputV, "-b.") % Vin versus time
hold on
plot(vecTime, vecOutputV, "-r.") % Vo versus time
hold off
title("Transient simulation for a step input")
xlabel("Time (s)")
ylabel("Voltage (V)")
legend("vin versus time", "vo versus time")
grid on
% Frequency domain plot (fft)
subplot(1,2,2)
% Calculate sampling frequency
Fs = 1/deltaT;
df = Fs/length(vecInputV);
vecFreqPlot = -Fs/2:df:Fs/2-df; % Create the frequency vector for plot
vecOmega = 2*pi*vecFreqPlot; % calculate the omega vector
fftvin = 20*log10(abs(fftshift(fft(vecInputV)))/simSteps); % Input fft in dB
plot(vecOmega, fftvin, "-b.") % Plot the input fft
hold on
fftvo = 20*log10(abs(fftshift(fft(vecOutputV)))/simSteps); % Output fft in dB
plot(vecOmega, fftvo, "-r.") % Plot the output fft
hold off
title("FFT of the step input")
xlabel("Omega (rad/s)")
ylabel("V (dB)")
legend("vin versus time", "vo versus time")
grid on
snapnow

```

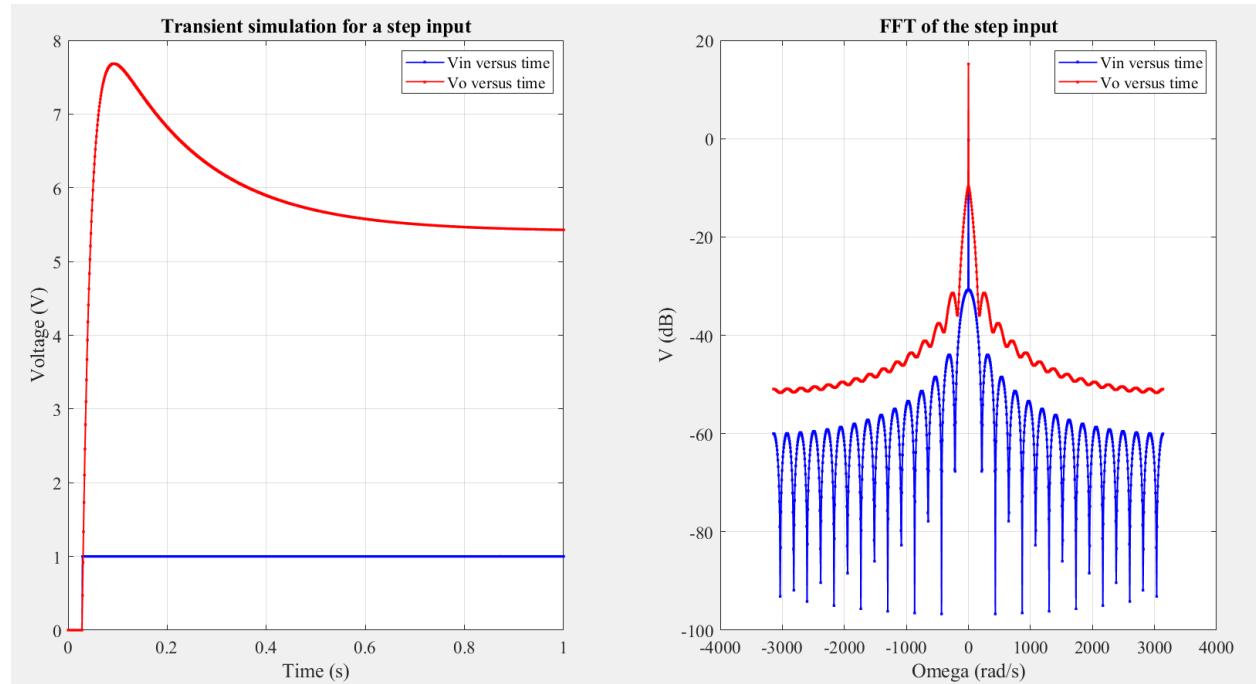


Figure 7 Transient simulation and FFT for a step input

Q4 d) Input signal B:

The input signal is a $\sin(2\pi f t)$ function with $f=1/0.03$ Hz. Try few other frequencies.

iii. Plot the input V_{in} and output V as the simulation progresses.

iv. After the simulation is completed, use the `fft()` and `fftshift()` functions to plot the frequency of the input and output signals.

```
% Declare the input for a sin(2*pi*f*t) with freq=1/0.03 Hz
freq = 1/0.03; % Hz
vecInputV = sin(2*pi*freq*vecTime);
% Hold the output vector
vecOutputV = zeros(1, simSteps);

% Initialize the V and F vector
vectorV = zeros(9, 1); % solution vector: [N1, N2, N3, N4, N5, I1, IL, I3, I4]
vectorF = zeros(9, 1); % F vector: F(1) = VIN
% Construct the A matrix
matrixA = matrixC/deltaT + matrixG;

% Loop through the simulation
for isim = 1:simSteps
    % Update the F vector
    vectorF(1) = vecInputV(isim);
    % Update the V vector
    vectorV = matrixA^-1 * (matrixC * vectorV / deltaT + vectorF);
    % Save the output voltage
    vecOutputV(isim) = vectorV(5);
end

% Plot of completed transient simulation for sinusoidal input with f = 1/0.03 Hz
figure(8)
subplot(1,2,1)
plot(vecTime, vecInputV, "-b.") % Vin versus time
hold on
plot(vecTime, vecOutputV, "-r.") % Vo versus time
hold off
title("Transient simulation for sinusoidal input with f = 1/0.03 Hz")
xlabel("Time (s)")
ylabel("Voltage (V)")
legend("Vin versus time", "Vo versus time")
grid on
% Frequency domain plot (fft)
subplot(1,2,2)
% Calculate sampling frequency
Fs = 1/deltaT;
df = Fs/length(vecInputV);
vecFreqPlot = -Fs/2:df:Fs/2-df; % Create the frequency vector for plot
vecOmega = 2*pi*vecFreqPlot; % Calculate the omega vector
fftvin = 20*log10(abs(fftshift(fft(vecInputV))/simSteps)); % Input fft in dB
plot(vecOmega, fftvin, "-b.") % Plot the input fft
hold on
```

```

fftvo = 20*log10(abs(fftshift(fft(vecOutputV)))/simSteps); % Output fft in dB
plot(vecOmega, fftvo, "-r.") % Plot the output fft
hold off
title("FFT of the sinusoidal input with f = 1/0.03 Hz")
xlabel("Omega (rad/s)")
ylabel("V (dB)")
legend("vin versus time", "Vo versus time")
grid on
snapnow

```

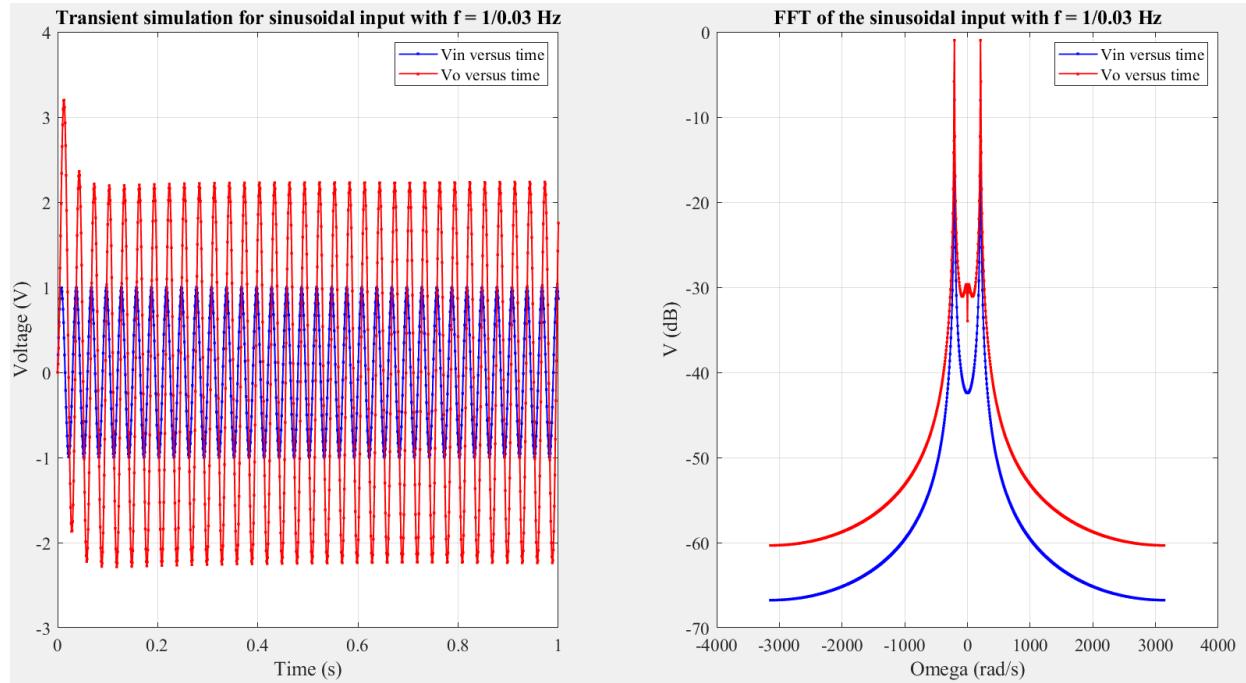


Figure 8 Transient simulation and the FFT for sinusoidal input with $f = 1/0.03 \text{ Hz}$

Q4 d) Input signal B (few other frequencies):

iii. Plot the input Vin and output V as the simulation progresses.

iv. After the simulation is completed, use the `fft()` and `fftshift()` functions to plot the frequency of the input and output signals.

```

% Declare the frequencies
vecFreq = [1, 10, 35]; % Hz

% Loop through the frequencies
for iFreq = 1:length(vecFreq)
    % Declare the input for a sin(2*pi*f*t)
    freq = vecFreq(iFreq); % Hz
    vecInputV = sin(2*pi*freq*vecTime);
    % Hold the output vector
    vecOutputV = zeros(1, simSteps);

    % Initialize the V and F vector

```

```

vectorV = zeros(9, 1); % solution vector: [N1, N2, N3, N4, N5, I1, IL, I3, I4]
vectorF = zeros(9, 1); % F vector: F(1) = VIN
% Construct the A matrix
matrixA = matrixC/deltaT + matrixG;

% Loop through the simulation
for isim = 1:simSteps
    % Update the F vector
    vectorF(1) = vecInputV(isim);
    % Update the V vector
    vectorV = matrixA^-1 * (matrixC * vectorV / deltaT + vectorF);
    % Save the output voltage
    vecOutputV(isim) = vectorV(5);
end

% Plot of completed transient simulation for sinusoidal input with f
figure(8+iFreq)
subplot(1,2,1)
plot(vecTime, vecInputV, "-b.") % Vin versus time
hold on
plot(vecTime, vecOutputV, "-r.") % Vo versus time
hold off
title("Transient simulation for sinusoidal input with f = "+freq+" Hz")
xlabel("Time (s)")
ylabel("Voltage (V)")
legend("Vin versus time", "Vo versus time")
grid on
% Frequency domain plot (fft)
subplot(1,2,2)
% Calculate sampling frequency
Fs = 1/deltaT;
df = Fs/length(vecInputV);
vecFreqPlot = -Fs/2:df:Fs/2-df; % Create the frequency vector for plot
vecOmega = 2*pi*vecFreqPlot; % Calculate the omega vector
fftvin = 20*log10(abs(fftshift(fft(vecInputV)))/simSteps); % Input fft in dB
plot(vecOmega, fftvin, "-b.") % Plot the input fft
hold on
fftvo = 20*log10(abs(fftshift(fft(vecOutputV)))/simSteps); % Output fft in dB
plot(vecOmega, fftvo, "-r.") % Plot the output fft
hold off
title("FFT of the sinusoidal input with f = "+freq+" Hz")
xlabel("Omega (rad/s)")
ylabel("V (dB)")
legend("vin versus time", "vo versus time")
grid on
snapnow
end

```

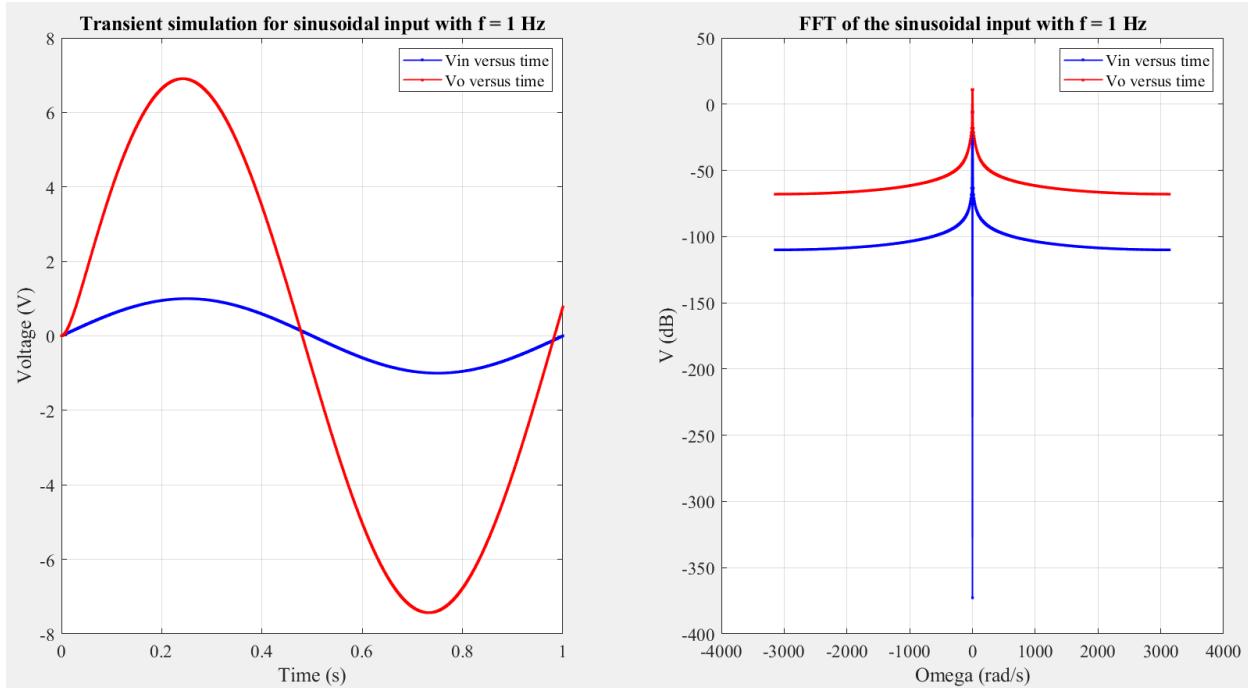


Figure 9 Transient simulation and the FFT for sinusoidal input with $f = 1$ Hz

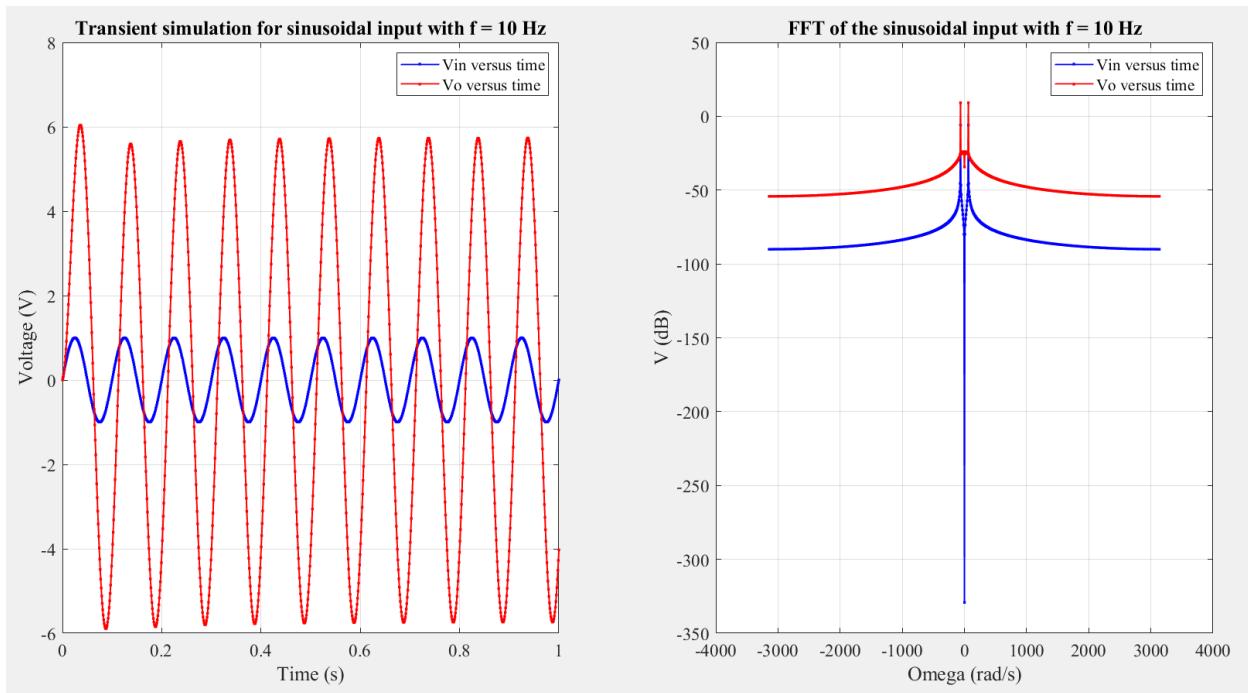


Figure 10 Transient simulation and the FFT for sinusoidal input with $f = 10$ Hz

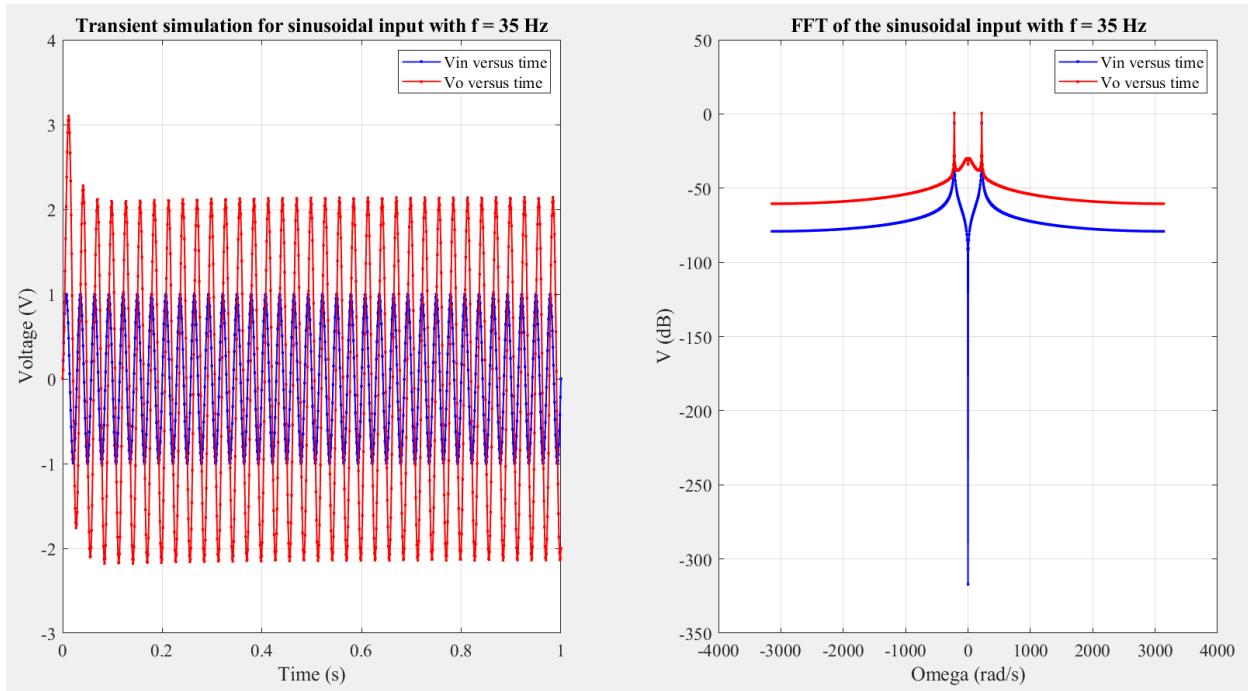


Figure 11 Transient simulation and the FFT for sinusoidal input with $f = 35$ Hz

As the frequency increases, the transient simulation plot is more crowded, and the two spikes in the FFT plot is separated further. This is expected because the Fourier Transform of a sine function is two Dirac Delta function as shown in follow:

$$\sin(2\pi f_o t) = \frac{e^{j2\pi f_o t} - e^{-j2\pi f_o t}}{2j}$$

$$\text{Fourier Transform } \{\sin(2\pi f_o t)\} = \frac{1}{2j} [\delta(f - f_o) - \delta(f + f_o)]$$

Therefore, as the frequency increases, the two spiles in the FFT plot are separated further. It should also be noted that if the frequency is too large without increasing the sampling rate (decreasing ΔT), there will be more error in the waveform.

Q4 d) Input signal C

A gaussian pulse with a magnitude of 1, std dev. of 0.03s and a delay of 0.06s

iii. Plot the input Vin and output V as the simulation progresses.

iv. After the simulation is completed, use the `fft()` and `fftshift()` functions to plot the frequency of the input and output signals.

```
% Declare the input for a gaussian pulse
stddev = 0.03; % std dev. of 0.03s
pulseDelay = 0.06; % delay pf 0.06s
vecInputV = exp(-((vectime-pulseDelay)/stddev).^2/2);
% Hold the output vector
vecOutputV = zeros(1, simSteps);
```

```

% Initialize the V and F vector
vectorV = zeros(9, 1); % solution vector: [N1, N2, N3, N4, N5, I1, IL, I3, I4]
vectorF = zeros(9, 1); % F vector: F(1) = VIN
% Construct the A matrix
matrixA = matrixC/deltaT + matrixG;

% Loop through the simulation
for isim = 1:simSteps
    % Update the F vector
    vectorF(1) = vecInputV(isim);
    % Update the V vector
    vectorV = matrixA^-1 * (matrixC * vectorV / deltaT + vectorF);
    % Save the output voltage
    vecOutputV(isim) = vectorV(5);
end

% Plot of completed transient simulation for a gaussian pulse
figure(12)
subplot(1,2,1)
plot(vecTime, vecInputV, "-b.") % Vin versus time
hold on
plot(vecTime, vecOutputV, "-r.") % Vo versus time
hold off
title("Transient simulation for Gaussian pulse input")
xlabel("Time (s)")
ylabel("Voltage (V)")
legend("Vin versus time", "Vo versus time")
grid on
% Frequency domain plot (fft)
subplot(1,2,2)
% Calculate sampling frequency
Fs = 1/deltaT;
df = Fs/length(vecInputV);
vecFreqPlot = -Fs/2:df:Fs/2-df; % Create the frequency vector for plot
vecOmega = 2*pi*vecFreqPlot; % Calculate the omega vector
fftvin = 20*log10(abs(fftshift(fft(vecInputV)))/simSteps); % Input fft in dB
plot(vecOmega,fftvin, "-b.") % Plot the input fft
hold on
fftvo = 20*log10(abs(fftshift(fft(vecOutputV)))/simSteps); % Output fft in dB
plot(vecOmega,fftvo, "-r.") % Plot the output fft
hold off
title("FFT of Gaussian pulse input")
xlabel("Omega (rad/s)")
ylabel("V (dB)")
legend("Vin versus time", "Vo versus time")
grid on
snapnow

```

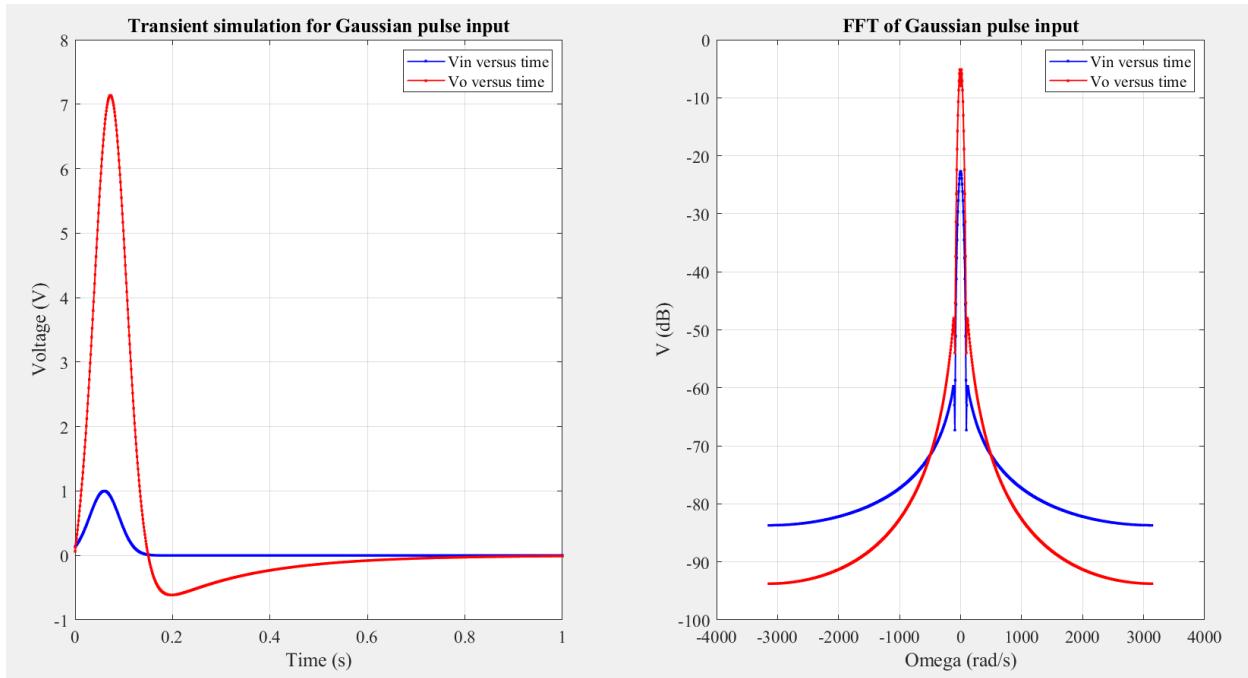


Figure 12 Transient simulation and the FFT for Gaussian pulse input

Q4 d) v

Increase the time step and see what happens. Comment.

The simulation steps are decreased to increase the time step (ΔT).

```

simTime = 1; % Simulate for 1 second
simSteps = 100; % Decrease the simulation steps to 100 steps
% calculate the deltaT
deltaT = simTime/simSteps; % second/step
% Declare the time vector
vectime = linspace(0,1,simSteps);

% Declare the input for a gaussian pulse
stddev = 0.03; % std dev. of 0.03s
pulseDelay = 0.06; % delay pf 0.06s
vecInputV = exp(-((vectime-pulseDelay)/stddev).^2/2);
% Hold the output vector
vecOutputV = zeros(1, simSteps);

% Initialize the v and F vector
vectorV = zeros(9, 1); % solution vector: [N1, N2, N3, N4, N5, I1, IL, I3, I4]
vectorF = zeros(9, 1); % F vector: F(1) = VIN
% Construct the A matrix
matrixA = matrixC/deltaT + matrixG;

% Loop through the simulation
for isim = 1:simSteps
    % Update the F vector
    vectorF(1) = vecInputV(isim);

```

```

% Update the v vector
vectorV = matrixA^-1 * (matrixC * vectorV / deltaT + vectorF);
% Save the output voltage
vecOutputV(isim) = vectorV(5);
end

% Plot of completed transient simulation for step input
figure(13)
% Time domain plot
subplot(1,2,1)
plot(vecTime, vecInputV, "-b.") % vin versus time
hold on
plot(vecTime, vecOutputV, "-r.") % vo versus time
hold off
title("Transient simulation for a Guassian input for "+ simSteps + " steps")
xlabel("Time (s)")
ylabel("Voltage (v)")
legend("vin versus time", "vo versus time")
grid on
% Frequency domain plot (fft)
subplot(1,2,2)
% Calculate sampling frequency
Fs = 1/deltaT;
df = Fs/length(vecInputV);
vecFreqPlot = -Fs/2:df:Fs/2-df; % Create the frequency vector for plot
vecOmega = 2*pi*vecFreqPlot; % Calculate the omega vector
fftVin = 20*log10(abs(fftshift(fft(vecInputV)))/simSteps); % Input fft in dB
plot(vecOmega,fftVin, "-b.") % Plot the input fft
hold on
fftVo = 20*log10(abs(fftshift(fft(vecOutputV)))/simSteps); % Output fft in dB
plot(vecOmega,fftVo, "-r.") % Plot the output fft
hold off
title("FFT of the Guassian input for "+simSteps+" steps")
xlabel("Omega (rad/s)")
ylabel("v (dB)")
legend("vin versus time", "vo versus time")
grid on
snapnow

```

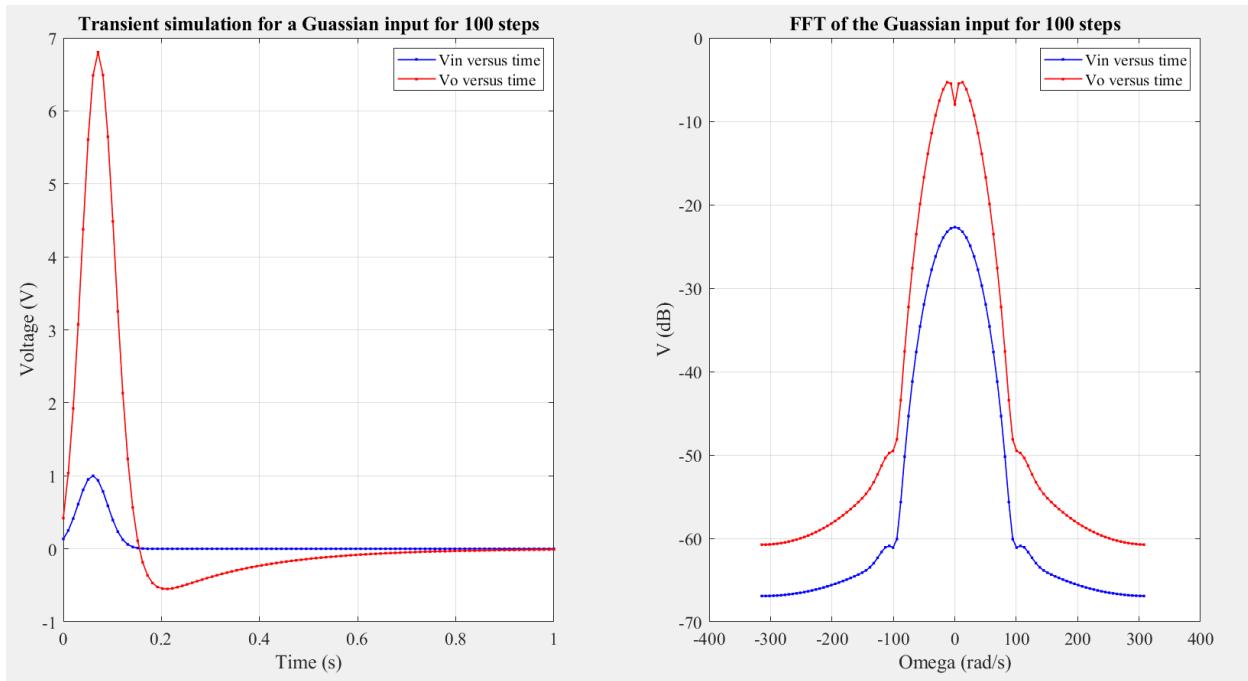


Figure 13 Transient simulation and the FFT for Gaussian pulse input with 100 simulation steps (increased ΔT)

Q4 d) v Comment

After increasing the time steps (decreases simulation steps), the time domain waveform contains less points, and the frequency domain plot contains less detail. This is because the sampling rate is lower.

Q5 Circuit with Noise

In Q5, a current source I_n in parallel with R3 is added to model the thermal noise generated in the resistor R3. A capacitor Cn in parallel with the resistor is also added to bandwidth limit the noise.

Please see Appendix B for the derivation and formulation of the matrices and equations.

```

simTime = 1; % Simulate for 1 second
simSteps = 1000; % use 1000 steps
% calculate the deltaT
deltaT = simTime/simSteps; % second/step
% Declare the time vector
vectime = linspace(0,1,simSteps);

% Declare the capacitor Cn
Cn = 0.00001;
magIn = 0.001; % Magnitude for IN

% Declare the input for a guassian pulse
stddev = 0.03; % std dev. of 0.03s
pulseDelay = 0.06; % delay pf 0.06s
vecInputV = exp(-((vectime-pulseDelay)/stddev).^2/2);
% Hold the output vector
vecOutputV = zeros(1, simSteps);

```

```

% Generate the vector for noise current
vecIn = magIn*randn(1, simSteps);

% Declare the vectors
vectorV = zeros(10, 1); % solution vector: [N1, N2, N3, N4, N5, I1, IL, I3, I4, In]
vectorF = zeros(10, 1); % F vector: F(1) = VIN, F(10) = IN

% Declare the C matrix
matrixC = [0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
            C, -C, 0, 0, 0, 0, 0, 0, 0, 0;
           -C, C, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, -L, 0, 0, 0;
            0, 0, cn, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0, 0];

% Declare the G matrix
matrixG = [1, 0, 0, 0, 0, 0, 0, 0, 0, 0;
            1/R1, -1/R1, 0, 0, 0, 1, 0, 0, 0, 0;
           -1/R1, 1/R1+1/R2, 0, 0, 0, 0, 1, 0, 0, 0;
            0, 1, -1, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, -1, 1, 0, 1;
            0, 0, -1/R3, 0, 0, 0, 0, 0, 0, 1, 0, 0;
            0, 0, 0, 1/R4, -1/R4, 0, 0, 0, 1, 0, 0;
            0, 0, 0, 1, 0, 0, 0, 0, -alpha, 0, 0;
            0, 0, 0, -1/R4, 1/R4+1/RO, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 1];

% Construct the A matrix
matrixA = matrixC/deltaT + matrixG;

% Loop through the simulation
for isim = 1:simSteps
    % Update the F vector for vin and In
    vectorF(1) = vecInputV(isim);
    vectorF(10) = vecIn(isim);
    % Update the V vector
    vectorV = matrixA^-1 * (matrixC * vectorV / deltaT + vectorF);
    % Save the output voltage
    vecOutputV(isim) = vectorV(5);
end

% Plot of completed transient simulation for a Gaussian input
figure(14)
% Time domain plot
subplot(1,2,1)
plot(vecTime, vecInputV, "-b.") % Vin versus time
hold on
plot(vecTime, vecOutputV, "-r.") % Vo versus time
hold off
title("Transient simulation for a Gaussian input with noise")

```

```

xlabel("Time (s)")
ylabel("Voltage (V)")
legend("vin versus time", "vo versus time")
grid on
% Frequency domain plot (fft)
subplot(1,2,2)
% Calculate sampling frequency
Fs = 1/deltaT;
df = Fs/length(vecInputV);
vecFreqPlot = -Fs/2:df:Fs/2-df; % Create the frequency vector for plot
vecOmega = 2*pi*vecFreqPlot; % calculate the omega vector
fftvin = 20*log10(abs(fftshift(fft(vecInputV)))/simSteps); % Input fft in dB
plot(vecOmega, fftvin, "-b.") % Plot the input fft
hold on
fftvo = 20*log10(abs(fftshift(fft(vecOutputV)))/simSteps); % output fft in dB
plot(vecOmega, fftvo, "-r.") % Plot the output fft
hold off
title("FFT of the Gaussian input with noise")
xlabel("Omega (rad/s)")
ylabel("V (dB)")
legend("vin versus time", "vo versus time")
grid on
snapnow

```

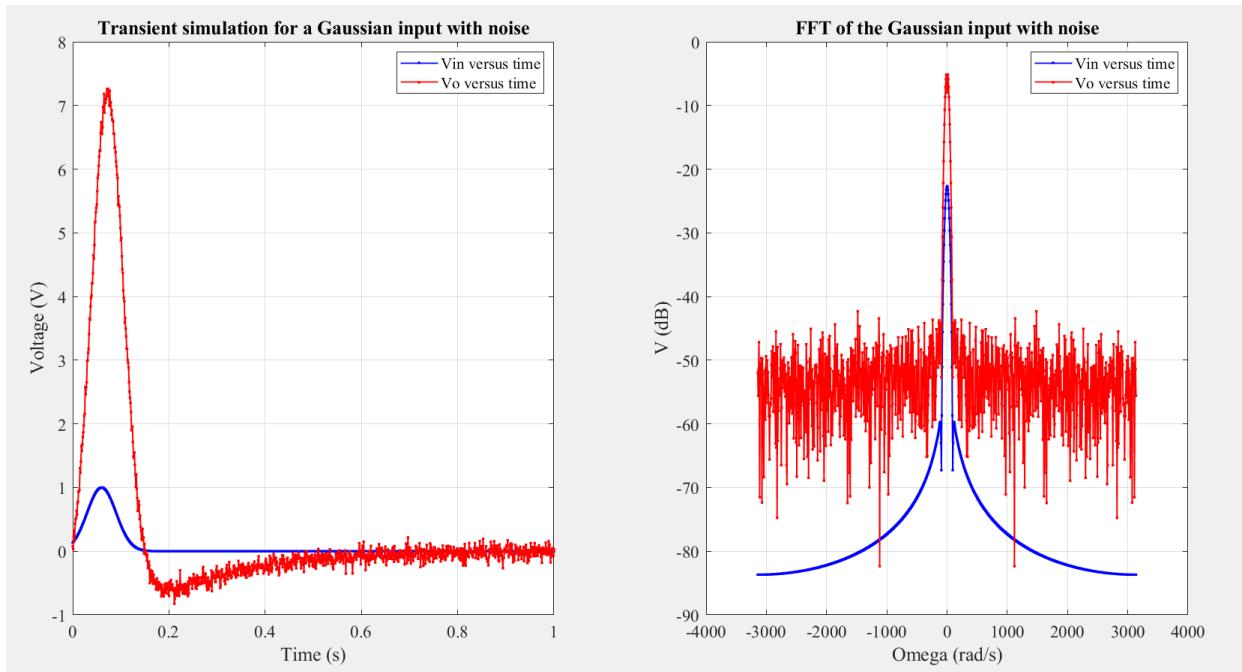


Figure 14 Transient simulation and the FFT for Gaussian pulse input with noise

Q5 vi

Vary C_n to see how the bandwidth changes. Comment on your results

```

% Create an array for three different Cn
arrCn = [0.000002, 0.0002, 0.02];

% Simulation loop for different Cn
for iCn = 1:length(arrCn)
    % Retrieve the corresponding Cn
    Cn = arrCn(iCn);
    magIn = 0.001; % Magnitude for In

    % Declare the input for a guassian pulse
    stdDev = 0.03; % std dev. of 0.03s
    pulseDelay = 0.06; % delay pf 0.06s
    vecInputV = exp(-((vectime-pulseDelay)/stdDev).^2/2);
    % Generate the vector for noise current
    vecIn = magIn*randn(1, simSteps);
    % Hold the output vector
    vecOutputV = zeros(1, simSteps);

    % Declare the vectors
    vectorV = zeros(10, 1); % solution vector: [N1, N2, N3, N4, N5, I1, IL, I3, I4, In]
    vectorF = zeros(10, 1); % F vector: F(1) = VIN, F(10) = In

    % Declare the C matrix
    matrixC = [0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               C, -C, 0, 0, 0, 0, 0, 0, 0, 0;
               -C, C, 0, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, -L, 0, 0, 0;
               0, 0, Cn, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0];
               0, 0, 0, 0, 0, 0, 0, 0, 0, 0];

    % Declare the G matrix
    matrixG = [1, 0, 0, 0, 0, 0, 0, 0, 0, 0;
               1/R1, -1/R1, 0, 0, 0, 1, 0, 0, 0, 0;
               -1/R1, 1/R1+1/R2, 0, 0, 0, 0, 1, 0, 0, 0;
               0, 1, -1, 0, 0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, -1, 1, 0, 1;
               0, 0, -1/R3, 0, 0, 0, 0, 1, 0, 0;
               0, 0, 0, 1/R4, -1/R4, 0, 0, 0, 1, 0;
               0, 0, 0, 1, 0, 0, 0, -alpha, 0, 0;
               0, 0, 0, -1/R4, 1/R4+1/R0, 0, 0, 0, 0, 0;
               0, 0, 0, 0, 0, 0, 0, 0, 0, 1];

    % Construct the A matrix
    matrixA = matrixC/deltaT + matrixG;

    % Loop through the simulation
    for isim = 1:simSteps
        % Update the F vector for Vin and In
        vectorF(1) = vecInputV(isim);

```

```

vectorF(10) = vecIn(isim);
% Update the V vector
vectorV = matrixA^-1 * (matrixC * vectorV / deltaT + vectorF);
% Save the output voltage
vecOutputV(isim) = vectorV(5);
end

% Plot of completed transient simulation for step input
figure(14+iCn)
% Time domain plot
subplot(1,2,1)
plot(vecTime, vecInputV, "-b.") % Vin versus time
hold on
plot(vecTime, vecoutputV, "-r.") % Vo versus time
hold off
title("Transient simulation for a Gaussian input with noise for Cn = "+Cn+" F")
xlabel("Time (s)")
ylabel("Voltage (V)")
legend("Vin versus time", "Vo versus time")
grid on
% Frequency domain plot (fft)
subplot(1,2,2)
% calculate sampling frequency
Fs = 1/deltaT;
df = Fs/length(vecInputV);
vecFreqPlot = -Fs/2:df:Fs/2-df; % Create the frequency vector for plot
vecOmega = 2*pi*vecFreqPlot; % calculate the omega vector
fftvin = 20*log10(abs(fftshift(fft(vecInputV)))/simSteps); % Input fft in dB
plot(vecOmega, fftvin, "-b.") % Plot the input fft
hold on
fftvo = 20*log10(abs(fftshift(fft(vecOutputV)))/simSteps); % Output fft in dB
plot(vecOmega, fftvo, "-r.") % Plot the output fft
hold off
title("FFT of the Gaussian input with noise for Cn = "+Cn+" F")
xlabel("Omega (rad/s)")
ylabel("V (dB)")
legend("vin versus time", "vo versus time")
grid on
snapnow
end

```

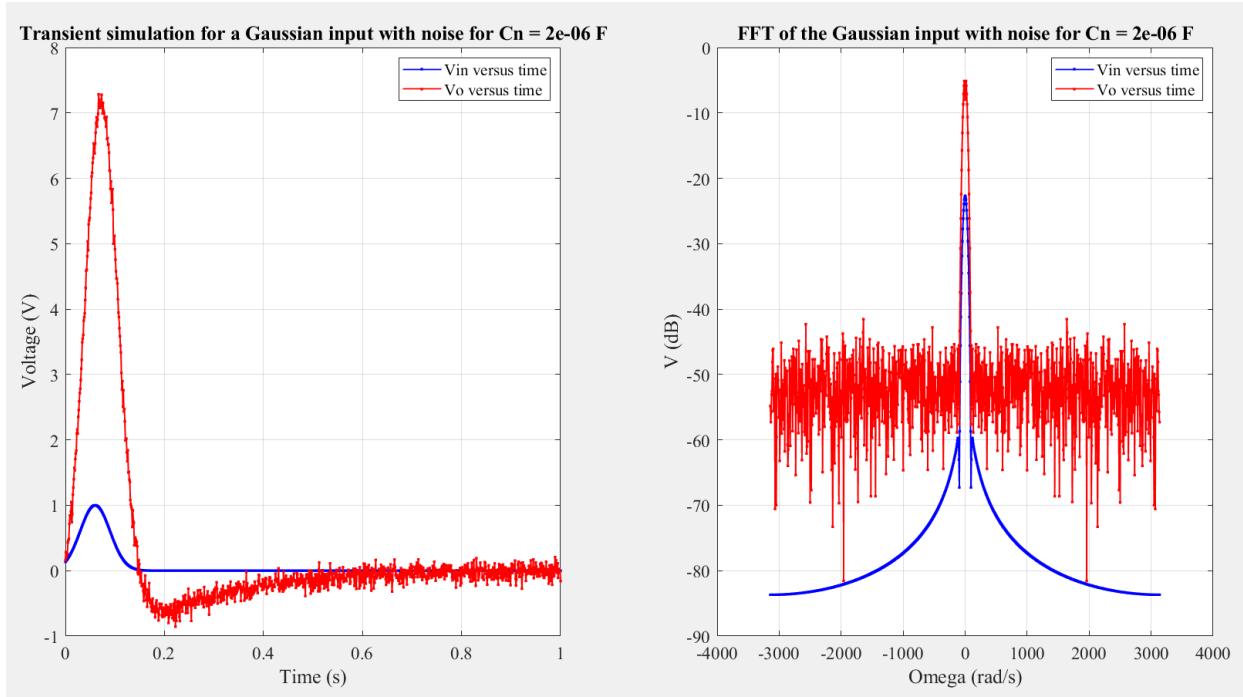


Figure 15 Transient simulation and the FFT for Gaussian pulse input with noise for $C_n = 2 \times 10^{-6} \text{ F}$

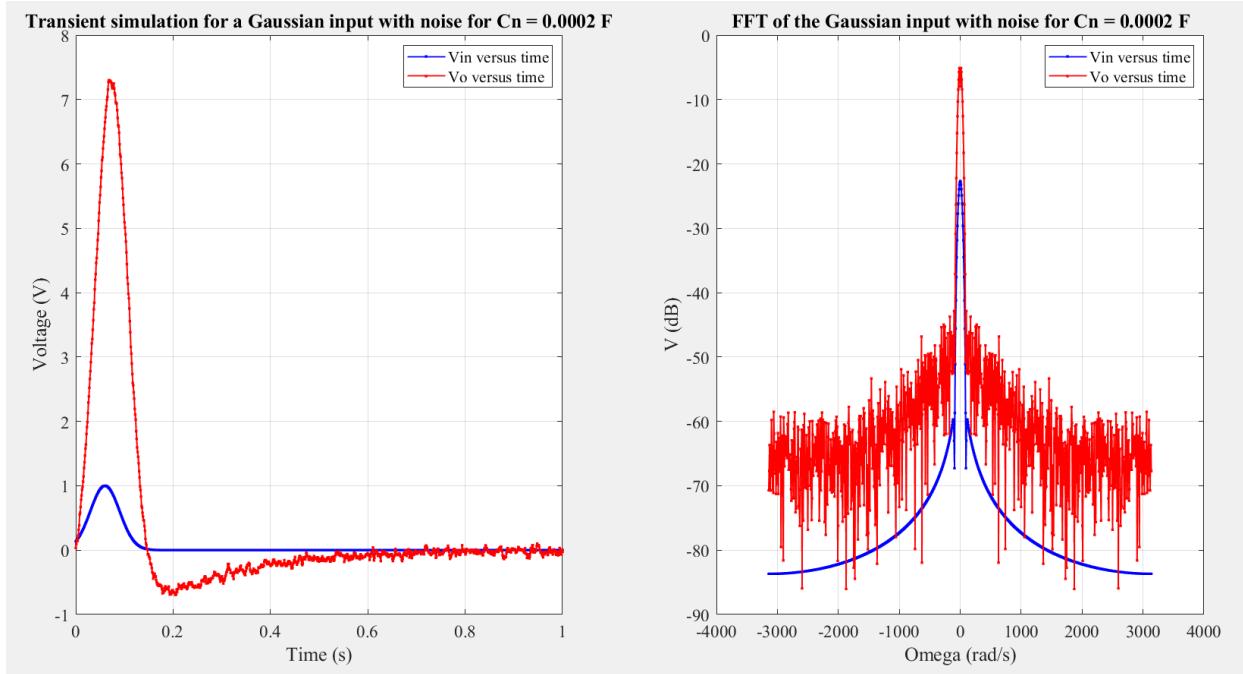


Figure 16 Transient simulation and the FFT for Gaussian pulse input with noise for $C_n = 0.0002 \text{ F}$

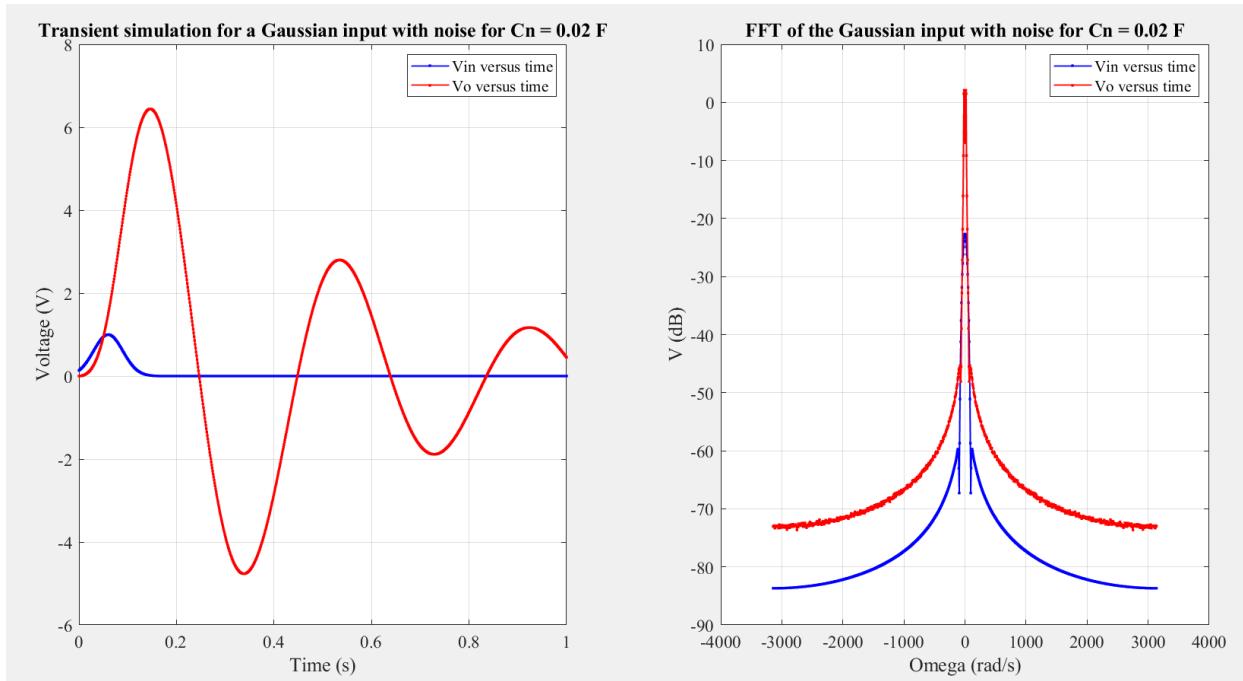


Figure 17 Transient simulation and the FFT for Gaussian pulse input with noise for $C_n = 0.02 \text{ F}$

Q5 vi. Comment

The bandwidth decreases as C_n increases. As C_n increases, and the output waveforms become smoother, which suggest that the effect of the noise is reduced. However, the transient output waveform for a large C_n value will also contain oscillations.

Q5 vii

Vary the time step and see how that changes the simulation.

In the following code, the simulation steps are varied, which effectively varied the time step since $\text{deltaT} = \text{simTime}/\text{simSteps}$, and simTime is 1 second.

```

simTime = 1; % Simulate for 1 second

% Create an array of simulation steps.
arrSimSteps = [100, 10000];
% Declare the capacitor Cn
Cn = 0.00001;
magIn = 0.001; % Magnitude for In

% Simulation loops for different simulation steps
for iSimSteps = 1:length(arrSimSteps)
    % Retrieve the simulation step
    simSteps = arrSimSteps(iSimSteps);
    % Calculate the deltaT
    deltaT = simTime/simSteps; % second/step
    % Declare the time vector
    vecTime = linspace(0,1,simSteps);

```

```

% Declare the input for a guassian pulse
stddev = 0.03; % std dev. of 0.03s
pulseDelay = 0.06; % delay pf 0.06s
vecInputV = exp(-((vecTime-pulseDelay)/stddev).^2/2);
% Generate the vector for noise current
vecIn = magIn*randn(1, simSteps);
% Hold the output vector
vecOutputV = zeros(1, simSteps);

% Declare the vectors
vectorV = zeros(10, 1); % solution vector: [N1, N2, N3, N4, N5, I1, IL, I3, I4, In]
vectorF = zeros(10, 1); % F vector: F(1) = VIN, F(10) = In

% Declare the C matrix
matrixC = [0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
           C, -C, 0, 0, 0, 0, 0, 0, 0, 0;
           -C, C, 0, 0, 0, 0, 0, 0, 0, 0;
           0, 0, 0, 0, 0, 0, -L, 0, 0, 0;
           0, 0, Cn, 0, 0, 0, 0, 0, 0, 0;
           0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
           0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
           0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
           0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
           0, 0, 0, 0, 0, 0, 0, 0, 0, 0];

% Declare the G matrix
matrixG = [1, 0, 0, 0, 0, 0, 0, 0, 0, 0;
           1/R1, -1/R1, 0, 0, 0, 1, 0, 0, 0, 0;
           -1/R1, 1/R1+1/R2, 0, 0, 0, 0, 1, 0, 0, 0;
           0, 1, -1, 0, 0, 0, 0, 0, 0, 0;
           0, 0, 0, 0, 0, 0, 0, -1, 1, 0, 1;
           0, 0, -1/R3, 0, 0, 0, 0, 0, 1, 0, 0;
           0, 0, 0, 1/R4, -1/R4, 0, 0, 0, 0, 1, 0, 0;
           0, 0, 0, 1, 0, 0, 0, 0, 0, -alpha, 0, 0;
           0, 0, 0, -1/R4, 1/R4+1/R0, 0, 0, 0, 0, 0, 0, 0;
           0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 1];

% Construct the A matrix
matrixA = matrixC/deltaT + matrixG;

% Loop through the simulation
for isim = 1:simSteps
    % Update the F vector for vin and In
    vectorF(1) = vecInputV(isim);
    vectorF(10) = vecIn(isim);
    % Update the V vector
    vectorV = matrixA^-1 * (matrixC * vectorV / deltaT + vectorF);
    % Save the output voltage
    vecOutputV(isim) = vectorV(5);
end

% Plot of completed transient simulation for step input
figure(18+isimSteps)
% Time domain plot

```

```

    subplot(1,2,1)
    plot(vecTime, vecInputV, "-b.") % Vin versus time
    hold on
    plot(vecTime, vecOutputV, "-r.") % Vo versus time
    hold off
    title("Transient simulation for a step input with noise for simulation steps = "+simSteps)
    xlabel("Time (s)")
    ylabel("Voltage (V)")
    legend("Vin versus time", "Vo versus time")
    grid on
    % Frequency domain plot (fft)
    subplot(1,2,2)
    % Calculate sampling frequency
    Fs = 1/deltaT;
    df = Fs/length(vecInputV);
    vecFreqPlot = -Fs/2:df:Fs/2-df; % Create the frequency vector for plot
    vecOmega = 2*pi*vecFreqPlot; % Calculate the omega vector
    fftvin = 20*log10(abs(fftshift(fft(vecInputV)))/simSteps); % Input fft in dB
    plot(vecOmega, fftvin, "-b.") % Plot the input fft
    hold on
    fftvo = 20*log10(abs(fftshift(fft(vecOutputV)))/simSteps); % Output fft in dB
    plot(vecOmega, fftvo, "-r.") % Plot the output fft
    hold off
    title("FFT of the step input with noise for simulation steps = "+simSteps)
    xlabel("Omega (rad/s)")
    ylabel("V (dB)")
    legend("Vin versus time", "Vo versus time")
    grid on
    snapnow
end

```

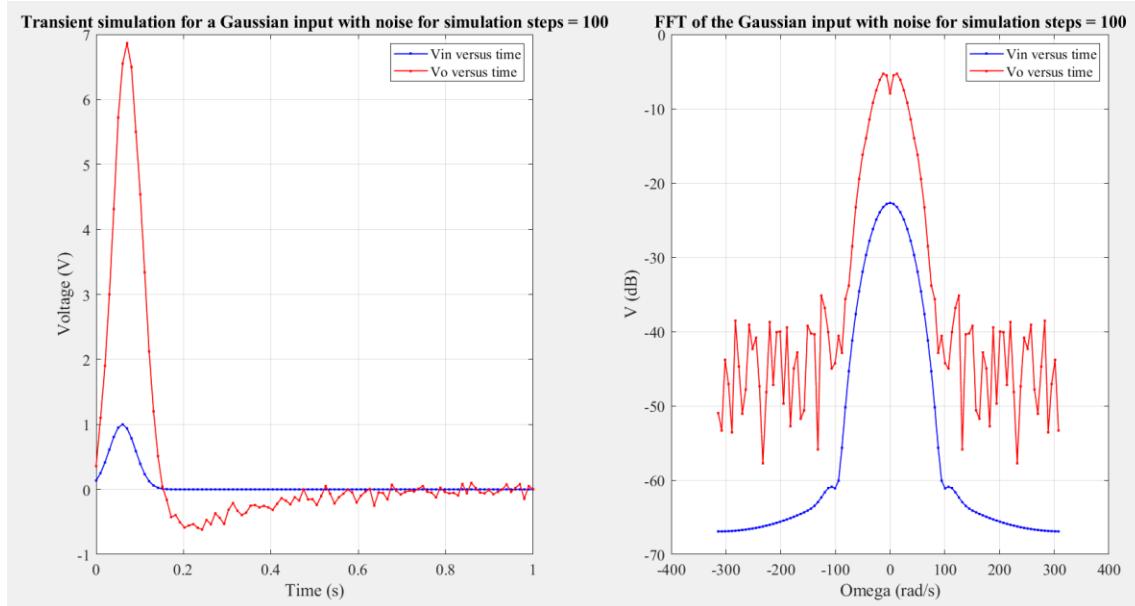


Figure 18 Transient simulation and the FFT for Gaussian pulse input with noise for simulation steps = 100 (large ΔT)

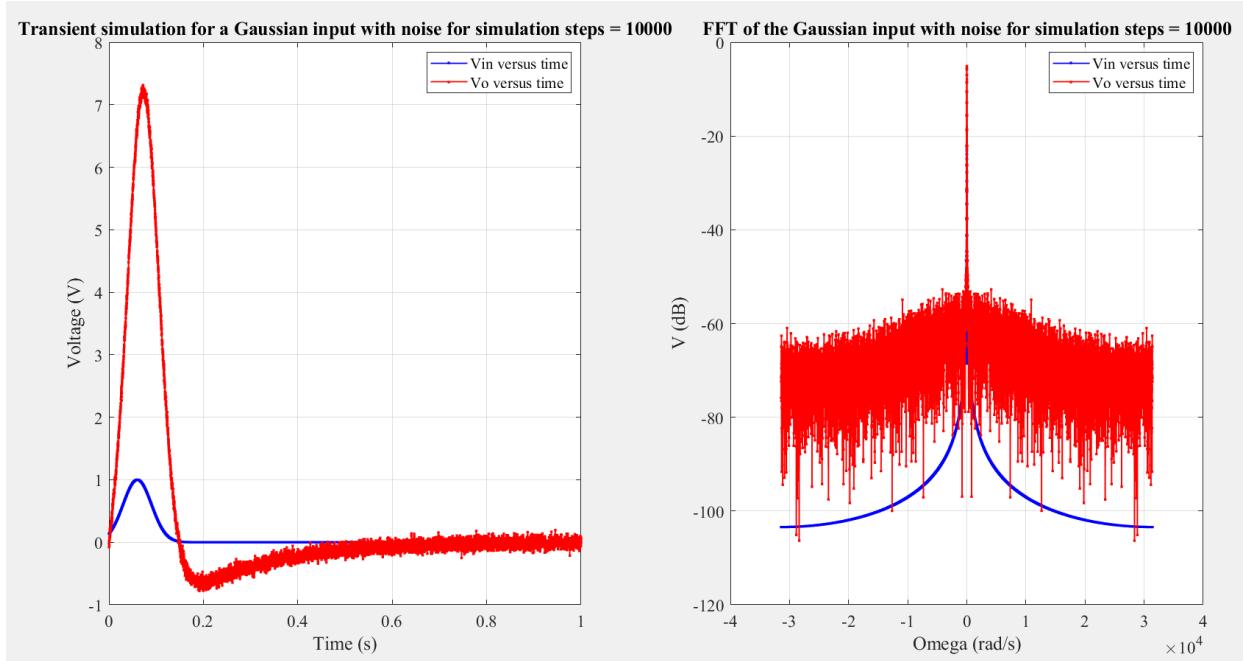


Figure 19 Transient simulation and the FFT for Gaussian pulse input with noise for simulation steps = 10000 (small ΔT)

Q5 vii Comment

The waveforms for large ΔT (low simulation steps) have less detail because the sampling rate is low, and the waveforms for small ΔT (higher simulation steps) have more detail because the sampling rate is high. The waveforms for the small ΔT show more details on the noise.

Q6 Non-linearity

If the voltage source on the output stage described by the transconductance equation $V = \alpha * I_3$ was instead modeled by $V = \alpha * I_3 + \beta * I_3^2 + \gamma * I_3^3$, what would need to change in your simulator?

To model the non-linearity, we can add a $B(V)$ vector in our matrix equation. The $B(V)$ vector models the non-linearity of the circuit: $V = \alpha I_3 + \beta I_3^2 + \gamma I_3^3$. The detail derivation is shown in the Appendix C. In each of the time step, we can use a loop implementing the Newton Raphson method to solve the non-linear matrix equation. The non-linear matrix equation is shown as follow:

$$C \frac{dV}{dt} + GV + B(V) = F(t)$$

To solve the non-linear matrix equation, the following steps are performed in a loop until dV is less than the tolerance:

1. Construct the $B(V)$ vector to model the non-linearity of the circuit
2. Compute $f(V_n) = \left(\frac{C}{\Delta t} + G \right) V_n - \frac{C}{\Delta t} V_{n-1} + B(V_n) - F(t)$
3. Compute the Jacobian matrix: $J = \frac{dB}{dV}$
4. Calculate the H matrix: $H = \frac{C}{\Delta t} + G + J$
5. Calculate $dV = -H^{-1}f(V_n)$

6. Update $V_n = V_n + dV$
 7. Check whether the tolerance is met or not

Q6 Implementation

The following code shows the implementation of the non-linearity.

```

-1/R1, 1/R1+1/R2, 0, 0, 0, 0, 0, 0, 0;
0, 1, -1, 0, 0, 0, 0, 0, 0;
0, 0, 0, 0, 0, 0, -1, 1, 0, 1;
0, 0, -1/R3, 0, 0, 0, 0, 0, 1, 0, 0;
0, 0, 0, 1/R4, -1/R4, 0, 0, 0, 1, 0, 0;
0, 0, 0, 1, 0, 0, 0, -alpha, 0, 0;
0, 0, 0, -1/R4, 1/R4+1/R0, 0, 0, 0, 0, 0, 0;
0, 0, 0, 0, 0, 0, 0, 0, 0, 1];

% Loop through the simulation
for iSim = 1:simSteps
    % Update the F vector for Vin and In
    vectorF(1) = vecInputV(iSim);
    vectorF(10) = vecIn(iSim);

    % Hold the old vectorV
    oldVectorV = vectorV;
    % Boolean indicating whether the tolerance is meet to end while loop
    bTolMeet = false;
    % Loop to find V vector
    while ~bTolMeet
        % Construct the B vector
        vectorB = zeros(10,1);
        vectorB(8) = -beta*vectorV(8)^2 - gamma*vectorV(8)^3;
        % Update the f(Vn) vector
        fvn = (matrixC/deltaT + matrixG)*vectorV - matrixC/deltaT*oldVectorV + vectorB - vectorF;
        % Construct the J matrix
        matrixJ = zeros(10,10);
        matrixJ(8, 8) = -2*beta*vectorV(8) - 3*gamma*vectorV(8)^2;
        % Calculate the H matrix
        matrixH = matrixC/deltaT + matrixG + matrixJ;
        % Calculate the deltv vector
        vecDeltaV = - matrixH^-1 * fvn;
        % Update the V vector
        vectorV = vectorV + vecDeltaV;
        % Check whether the tolerance is met or not
        bTolMeet = abs(vecDeltaV) <= tol;
    end

    % Save the output voltage
    vecOutputV(iSim) = vectorV(5);
end

% Plot of completed transient simulation for step input
figure(21)
% Time domain plot
subplot(1,2,1)
plot(vecTime, vecInputV, "-b.") % Vin versus time
hold on
plot(vecTime, vecOutputV, "-r.") % Vo versus time
hold off
title("Transient simulation for a sinusoidal input with noise and non-linearity")
xlabel("Time (s)")

```

```

ylabel("Voltage (V)")
Legend("vin versus time", "vo versus time")
grid on
% Frequency domain plot (fft)
subplot(1,2,2)
% Calculate sampling frequency
Fs = 1/deltaT;
df = Fs/length(vecInputV);
vecFreqPlot = -Fs/2:df:Fs/2-df; % Create the frequency vector for plot
vecOmega = 2*pi*vecFreqPlot; % calculate the omega vector
fftVin = 20*log10(abs(fftshift(fft(vecInputV))/simSteps)); % Input fft in dB
plot(vecOmega,fftVin, "-b.") % Plot the input fft
hold on
fftVo = 20*log10(abs(fftshift(fft(vecOutputV))/simSteps)); % Output fft in dB
plot(vecOmega,fftVo, "-r.") % Plot the output fft
hold off
title("FFT of a sinusoidal input with noise and non-linearity")
xlabel("Omega (rad/s)")
ylabel("V (dB)")
legend("vin versus time", "vo versus time")
grid on
snapnow

```

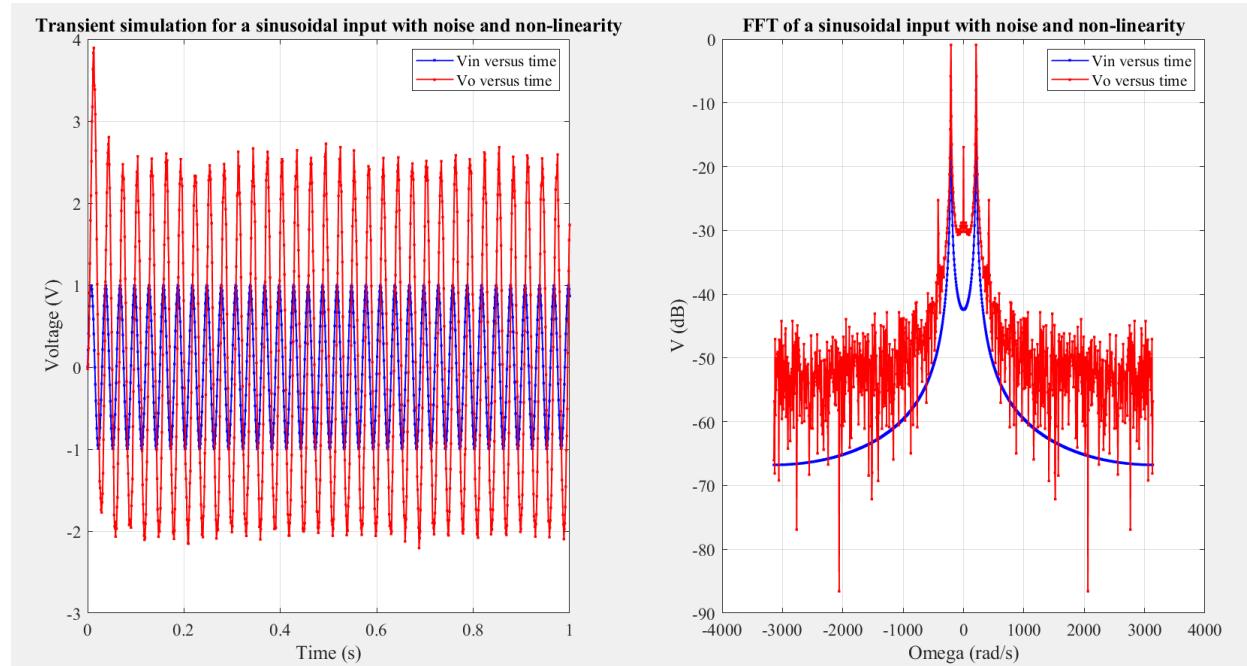


Figure 20 Transient simulation and the FFT for sinusoidal input with noise and non-linearity

The nonlinearity of the circuit is shown as the varying amplitude in transient simulation waveform, and the nonlinearity of the circuit is shown as spikes in the FFT waveform.

Helper functions

The following functions are helper functions used in the main code

```
% Helper function for mapping index
% @param iRow = i index for the row
%         jRow = j index for the column
%         ny   = size of the y
function [n] = mappingEq(iRow, jCol, ny)
    n = jCol + (iRow - 1) * ny;
end % End mappingEq

% Helper function to add the obstacles
% @ param boxLF = length of the box in fraction of region.x
%         boxWF = width of the box in fraction of region.y
%         region = region.x and region.y
function [numBox] = AddObstacles(boxLF, boxWF, region)
global boxes % Matrix for holding the boxes
% Find the x, y, w, h for the bottom box
xbb = region.x/2 - region.x*boxLF/2;
ybb = 0;
wbb = region.x*boxLF;
hbb = region.y * boxWF;
% Find the x, y, w, h for the upper box
xub = region.x/2 - region.x * boxLF/2;
yub = region.y * (1-boxWF);
wub = region.x * boxLF;
hub = region.y * boxWF;
% Create the boxes
boxes = [xbb ybb wbb hbb;
          xub yub wub hub];
% Return number of boxes
numBox = height(boxes);
end % End AddObstacles

% This function add a bunch of electrons in a given region randomly for Q3
% @param numE = number of electrons
%         region = region for the electrons
%         T = temperature in Kelvin
%         numBox = number of boxes
function AddElectrons_withBox(numE, region, T, numBox)
global Const % Constants
global x y % arrays for current electron positions
global xp yp % arrays for previous electron positions
global vx vy % arrays for current electron velocities
global boxes % Matrix for the boxes position

% Create the arrays for electrons locations
x = rand(1, numE) * region.x;
y = rand(1, numE) * region.y;
```

```


% Loop through the electrons to make sure that no electrons inside obstacles
for iE = 1:numE
    % Flag to indicate whether inside box
    insideBox = true;
    while (insideBox)
        insideBox = false;
        % Loop through the boxes
        for iBox = 1:numBox
            % Check for invalid electrons position
            if (x(iE)>boxes(iBox, 1) && x(iE)<(boxes(iBox, 1)+boxes(iBox, 3)) ...
                && y(iE)>boxes(iBox, 2) && y(iE) < (boxes(iBox, 2)+boxes(iBox, 4)))
                insideBox = true;
                break;
            end
        end
        if (insideBox)
            % Regenerate position
            x(iE) = rand() * region.x;
            y(iE) = rand() * region.y;
        end
    end
end
% Create the arrays for previous electron positions
xp = x;
yp = y;
% Create helper arrays for velocity distribution
vx = sqrt(Const.kb*T/Const.mn).*randn(1, numE);
vy = sqrt(Const.kb*T/Const.mn).*randn(1, numE);
end % End AddElectrons_WithBox

```

Published with MATLAB® R2021b

Appendix A

ELEC 4700 NNA Building.

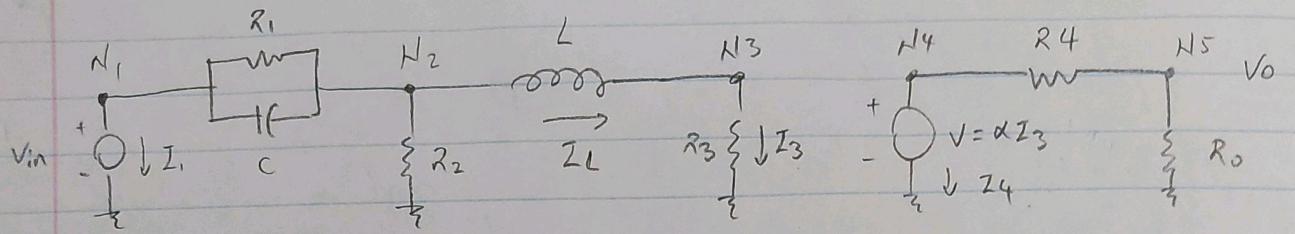

(a) node N_1 : $[N_1 = V_{in}]$

$$I_1 + \frac{N_1 - N_2}{R_1} + C \frac{\partial(N_1 - N_2)}{\partial t} = 0$$

node N_2 : $\left[\frac{N_2 - N_1}{R_1} + C \frac{\partial(N_2 - N_1)}{\partial t} + \frac{N_2}{R_2} + I_L = 0 \right]$
 $N_2 - N_3 = L \frac{\partial I_L}{\partial t}$

node N_3 : $[-I_L + I_3 = 0]$

$$I_3 = \frac{N_3}{R_3}$$

node N_4 : $\left[I_4 + \frac{N_4 - N_5}{R_4} = 0 \right] \quad [N_4 = \alpha I_3]$

node N_5 :

$$\left[\frac{N_5 - N_4}{R_4} + \frac{N_5}{R_0} = 0 \right]$$

$$V_0 = N_5$$

$$C \frac{\partial \vec{V}}{\partial t} + G \vec{V} = \vec{F}$$

(2)

$V(9 \times 1) \quad F(9 \times 1)$
 $C(9 \times 9) \quad G(9 \times 9)$
 \wedge capacitor, L.

$$\textcircled{1} \quad N_1 = V_{IN}$$

$$\textcircled{2} \quad C \frac{\partial N_1}{\partial t} - C \frac{\partial N_2}{\partial t} + -\frac{1}{R_1} N_1 - \frac{1}{R_1} N_2 + I_1 = 0$$

$$\textcircled{3} \quad -C \frac{\partial N_1}{\partial t} + C \frac{\partial N_2}{\partial t} + -\frac{1}{R_1} N_1 + \left(\frac{1}{R_1} + \frac{1}{R_2}\right) N_2 + I_2 = 0$$

$$\textcircled{4} \quad -L \frac{\partial I_L}{\partial t} + N_2 - N_3 = 0$$

$$\textcircled{5} \quad -I_L + I_3 = 0$$

$$\textcircled{6} \quad -\frac{1}{R_3} N_3 + I_3 = 0$$

$$\textcircled{7} \quad \frac{1}{R_4} N_4 - \frac{1}{R_4} N_5 + I_4 = 0$$

$$\textcircled{8} \quad N_4 - \alpha I_3 = 0$$

$$\textcircled{9} \quad -\frac{1}{R_4} N_4 + \left(\frac{1}{R_4} + \frac{1}{R_5}\right) N_5 = 0$$


$$\vec{V} = \begin{bmatrix} N_1 \\ N_2 \\ N_3 \\ N_4 \\ N_5 \\ I_1 \\ I_L \\ I_3 \\ I_4 \end{bmatrix} \quad \vec{F} = \begin{bmatrix} V_{IN} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad C = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ C & -C & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ -C & C & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & -L & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$G = \begin{bmatrix} N_1 & N_2 & N_3 & N_4 & N_5 & I_1 & I_2 & I_3 & I_4 \\ 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ \frac{1}{R_1} & -\frac{1}{R_1} & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 \\ 0 & 0 & -\frac{1}{R_3} & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & \frac{1}{R_4} & -\frac{1}{R_4} & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & -\alpha & 0 \\ 0 & 0 & 0 & -\frac{1}{R_4} & \frac{1}{R_4} + \frac{1}{R_0} & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$C \frac{\partial \vec{V}}{\partial t} + G \vec{V} = \vec{F}$$

$$(G + j\omega C) \vec{V} = \vec{F}(w)$$

Appendix B Circuit with noise source

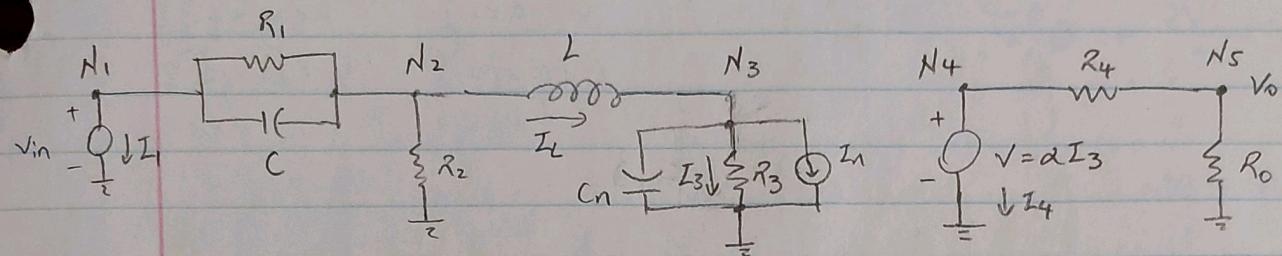

node N_1 : $| N_1 = V_{in} |$

$$\boxed{I_1 + \frac{N_1 - N_2}{R_1} + C \frac{\partial(N_1 - N_2)}{\partial t} = 0}$$

node N_2 : $\boxed{\frac{N_2 - N_1}{R_1} + C \frac{\partial(N_2 - N_1)}{\partial t} + \frac{N_2}{R_2} + I_L = 0}$

$$\boxed{N_2 - N_3 = L \frac{\partial I_L}{\partial t}}$$

node N_3 : $\boxed{-I_L + I_3 + I_n + C_n \frac{\partial N_3}{\partial t} = 0}$

$$\boxed{I_3 = \frac{N_3}{R_3}}$$

$$\boxed{I_n = I_n}$$

node N_4 : $\boxed{I_4 + \frac{N_4 - N_5}{R_4} = 0}$ $\boxed{N_4 = \alpha I_3}$

node N_5 : $\boxed{\frac{N_5 - N_4}{R_4} + \frac{N_5}{R_0} = 0}$

$$\boxed{V_o = N_5}$$

$$\left(\frac{\partial \vec{V}}{\partial t} + G \vec{V} \right) = \vec{F}$$

$V(10 \times 1)$ $F(10 \times 1)$
 (10×10) $G(10 \times 10)$

$$\textcircled{1} \quad n_1 = v_{in}$$

$$\textcircled{2} \quad C \frac{\partial N_1}{\partial t} - C \frac{\partial N_2}{\partial t} + \frac{1}{R_1} N_1 - \frac{1}{R_2} N_2 + I_1 = 0$$

$$③ -C \frac{\partial N_1}{\partial t} + C \frac{\partial N_2}{\partial t} + -\frac{1}{R_1} N_1 + \left(\frac{1}{R_1} + \frac{1}{R_2} \right) N_2 + I_L = 0$$

$$④ -L \frac{\partial I_L}{\partial t} + N_2 - N_3 = 0$$

$$\textcircled{5} \quad C_n \frac{\partial N_3}{\partial t} - I_L + I_3 + I_n = 0$$

$$⑥ - \frac{1}{R_3} N_3 + I_3 = 0$$

$$\textcircled{1} \quad \frac{1}{R_4} N_4 - \frac{1}{R_4} N_5 + I_4 = 0$$

$$⑧ N_4 - \alpha I_3 = 0$$

$$⑨ - \frac{1}{R_4} N_4 + \left(\frac{1}{R_4} + \frac{1}{R_0} \right) N_5 = 0$$

$$⑩ \quad I_n = I_n$$

$N_1 \quad N_2 \quad N_3 \quad N_4 \quad N_5 \quad I_1 \quad I_2 \quad I_3 \quad I_4 \quad I_5$

$$\vec{V} = \begin{bmatrix} N_1 \\ N_2 \\ N_3 \\ N_4 \\ N_5 \\ I_1 \\ I_L \\ I_3 \\ I_4 \\ I_n \end{bmatrix} \quad \vec{F} = \begin{bmatrix} V_{in} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ I_n \end{bmatrix}$$

(3)

$$G = \begin{bmatrix} N_1 & N_2 & N_3 & N_4 & N_5 & I_1 & I_L & I_3 & I_4 & I_n \\ 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ \frac{1}{R_1} & -\frac{1}{R_1} & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 1 \\ 0 & 0 & -\frac{1}{R_3} & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{R_4} & -\frac{1}{R_4} & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & -\alpha & 0 & 0 \\ 0 & 0 & 0 & -\frac{1}{R_4} & \frac{1}{R_4} + \frac{1}{R_0} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$


$$C \frac{d\vec{V}}{dt} + G \vec{V} = \vec{F}$$

$$(G + j\omega C) \vec{V} = \vec{F}(\omega)$$

Time Domain :

$$\vec{V}^j = A^{-1} \left[\left(\frac{\vec{V}^{j-1}}{j\omega} + \vec{F}(t^j) \right) \right] \text{ where } A = \frac{C}{j\omega} + G$$

Appendix C Nonlinearity

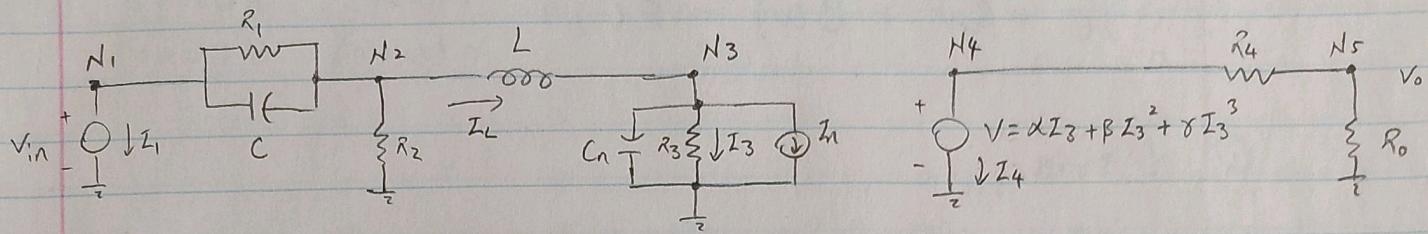

$$\text{node } N_1 : \boxed{N_1 = V_{in}}$$

$$\boxed{I_1 + \frac{N_1 - N_2}{R_1} + C \frac{\partial(N_1 - N_2)}{\partial t} = 0}$$

$$\text{node } N_2 : \boxed{\frac{N_2 - N_1}{R_1} + C \frac{\partial(N_2 - N_1)}{\partial t} + \frac{N_2}{R_2} + I_L = 0}$$

$$\boxed{N_2 - N_3 = L \frac{\partial I_L}{\partial t}}$$

node N_3 :

$$\boxed{-I_L + I_3 + I_n + C_n \frac{\partial N_3}{\partial t} = 0}$$

$$\boxed{I_3 = \frac{N_3}{R_3}}$$

$$\boxed{I_n = I_n}$$

node N_4

$$\boxed{I_4 + \frac{N_4 - N_5}{R_4} = 0}$$

$$\boxed{N_4 = \alpha I_3 + \beta I_3^2 + \gamma I_3^3}$$

node N_5 :

$$\boxed{\frac{N_5 - N_4}{R_4} + \frac{N_5}{R_0} = 0}$$

$$\boxed{V_o = N_5}$$

$$(\frac{\partial \vec{v}}{\partial t} + G\vec{v} + \vec{B}(v) = \vec{F}(t) \quad \begin{matrix} v(10 \times 1) \\ C(10 \times 10) \end{matrix} \quad \begin{matrix} F(10 \times 1) \\ G(10 \times 10) \end{matrix} \quad \begin{matrix} B(10 \times 1) \end{matrix})$$

$$\textcircled{1} \quad N_1 = \sqrt{\nu n}$$

$$② C \frac{\partial N_1}{\partial t} - C \frac{\partial N_2}{\partial t} + \frac{1}{R_1} N_1 - \frac{1}{R_1} N_2 + I_1 = 0$$

$$③ -C \frac{\partial N_1}{\partial t} + C \frac{\partial N_2}{\partial t} + -\frac{1}{R_1} N_1 + \left(\frac{1}{R_1} + \frac{1}{R_2} \right) N_2 + I_L = 0$$

$$④ -L \frac{\partial I_L}{\partial t} + N_2 - N_3 = 0$$

$$⑤ C_n \frac{\partial N_3}{\partial t} - I_L + I_3 + I_n = 0$$

$$⑥ -\frac{1}{R_3} N_3 + I_3 = 0$$

$$⑦ \quad -\frac{1}{R_4} N_4 - \frac{1}{R_4} N_5 + I_4 = 0$$

$$(8) \quad N_4 - \alpha I_3 - \beta I_3^2 - \gamma I_3^3 = 0$$

$$⑨ -\frac{1}{R_4} N_4 + \left(\frac{1}{R_4} + \frac{1}{R_0} \right) N_5 = 0$$

$$\textcircled{10} \quad I_n = I_n$$

3

$$C \frac{\vec{v}}{\Delta t} + G \vec{v} + \vec{B}(v_n) = \vec{F}(t)$$

$$(\frac{\vec{v}_n - \vec{v}_{n-1}}{\Delta t} + G \vec{v}_n + \vec{B}(v_n) = \vec{F}(t))$$

$$\underbrace{\left(\frac{C}{\Delta t} + G \right) \vec{v}_n - \frac{C}{\Delta t} \vec{v}_{n-1} + \vec{B}(v_n) - \vec{F}(t) }_{f(\vec{v})} = 0$$

$$\therefore f(\vec{v} + d\vec{v}) \approx f(\vec{v}) + \frac{\partial f}{\partial v} dv = 0$$

$$\therefore dv = - \left[\frac{\partial f}{\partial v} \right]^{-1} f(\vec{v})$$

$$f(\vec{v}) = \left(\frac{C}{\Delta t} + G \right) \vec{v}_n - \frac{C}{\Delta t} \vec{v}_{n-1} + \vec{B}(v_n) - \vec{F}(t)$$

$$\text{let } H = \frac{\partial f}{\partial v} = \frac{C}{\Delta t} + G + J, \text{ where } J = \frac{\partial B}{\partial v}$$

Iterate while $dV > tol$

$$f(v_n) = \left(\frac{C}{\Delta t} + G \right) \vec{v}_n - \frac{C}{\Delta t} \vec{v}_{n-1} + \vec{B}(v_n) - \vec{F}(t)$$

$$\vec{H} = \frac{C}{\Delta t} + G + J$$

$$d\vec{v} = - H^{-1} f(v_n)$$

$$\vec{v}_n = \vec{v}_n + d\vec{v}$$